



# Выбор понижающих DC/DC преобразователей в зависимости от особенностей архитектуры и применения


Ralf Regenhold

Dmitri Yablokov

# **Методы стабилизации (особенности петли ОС)**


**Методы достижения наилучшего результата  
при различных требованиях**

# На что влияют методы стабилизации?

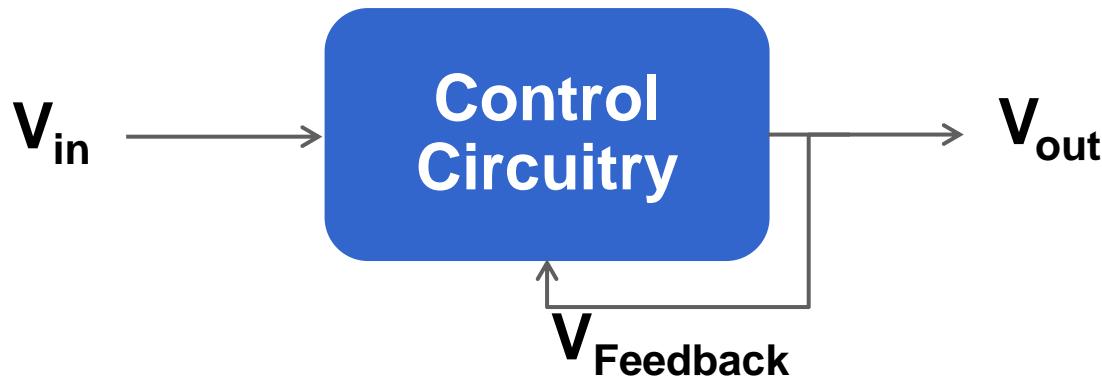

- Архитектура – метод стабилизации напряжения (тока)
- Качество стабилизации
  - Скорость реакции на переходные процессы (Transient performance)
  - Фиксированная/ плавающая частота (влияние на EMI)
  - Возможности синхронизации (in multi stage systems)
  - Пульсации и стабильность выходного напряжения
- Стоимость полного решения
- Сложность разработки
  - Стабильность петли ОС (compensation network)

# Hysteretic Control Architectures

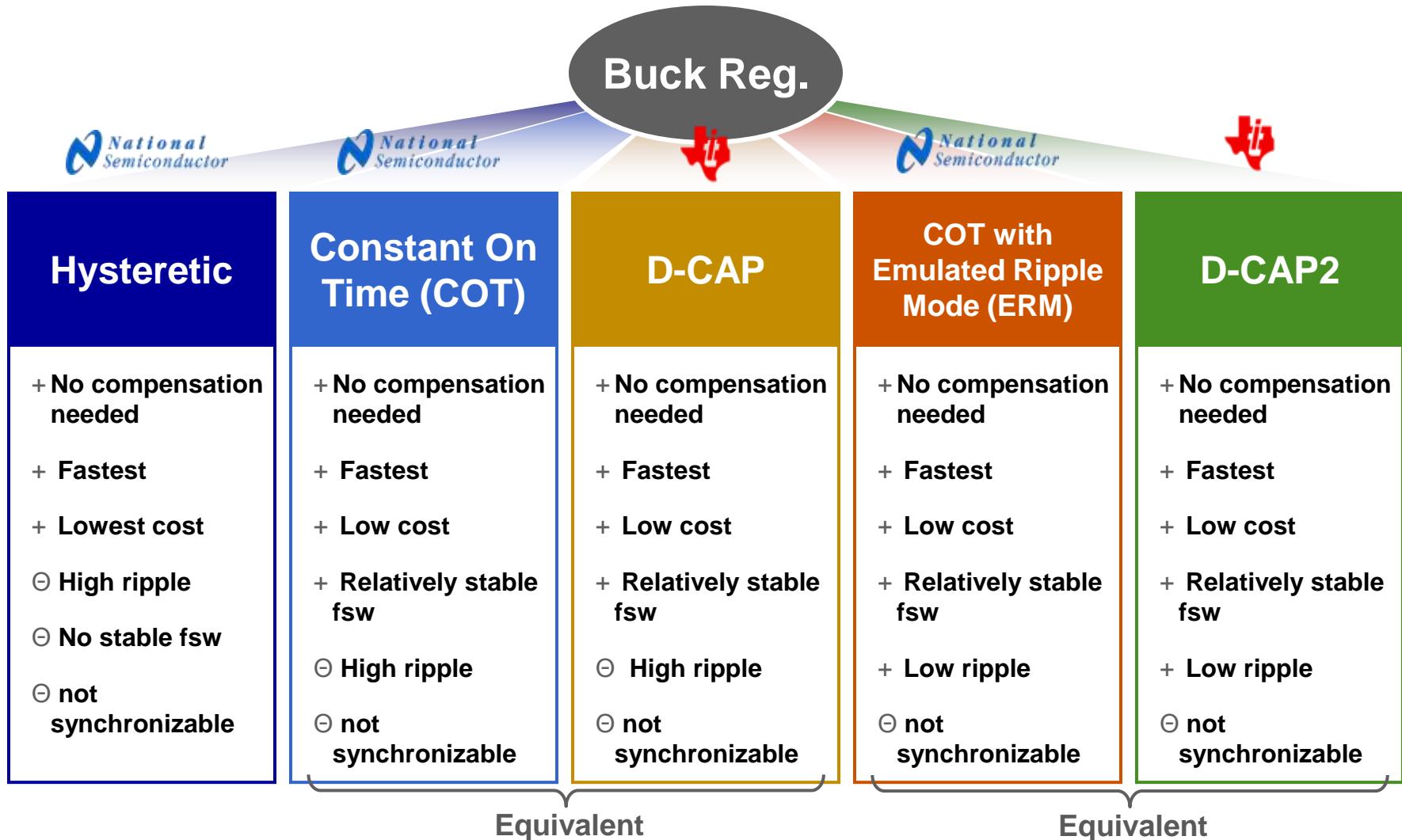

# Fixed Frequency Control Architectures


Buck Reg.

Voltage Mode	Voltage Mode with Vin feed forward	Current Mode	Emulated Current Mode	DCS-Control
<ul style="list-style-type: none"><li>+ Stable fsw</li><li>+ Low ripple</li><li>+ Synchronizable</li><li>+ Wide duty cycle range</li><li>+ Medium cost</li><li>- Slow Transient</li><li>- Complex compensation needed</li></ul>	<ul style="list-style-type: none"><li>+ Stable fsw</li><li>+ Low ripple</li><li>+ Synchronizable</li><li>+ Medium cost</li><li>+ Compensates Vin changes</li><li>+ Fast Transient</li><li>- Complex compensation needed</li></ul>	<ul style="list-style-type: none"><li>+ Stable fsw</li><li>+ Low ripple</li><li>+ Synchronizable</li><li>+ Fast Transient</li><li>+ Simple compensation</li><li>+ Compensates Vin changes</li><li>- No low duty cycle</li><li>- Higher cost</li></ul>	<ul style="list-style-type: none"><li>+ Stable fsw</li><li>+ Low ripple</li><li>+ Synchronizable</li><li>+ Fast Transient</li><li>+ Simple compensation</li><li>+ Compensates Vin changes</li><li>- No high duty cycle</li><li>- Higher cost</li></ul>	<ul style="list-style-type: none"><li>+ Fastest</li><li>+ Advanced Power Safe Mode</li><li>+ Low ripple</li><li>+ Relatively stable fsw</li><li>+ Low BOM cost</li><li>- not synchronizable</li></ul>

# **Hysteretic Mode Regulation**

**Наименьшее время отклика**
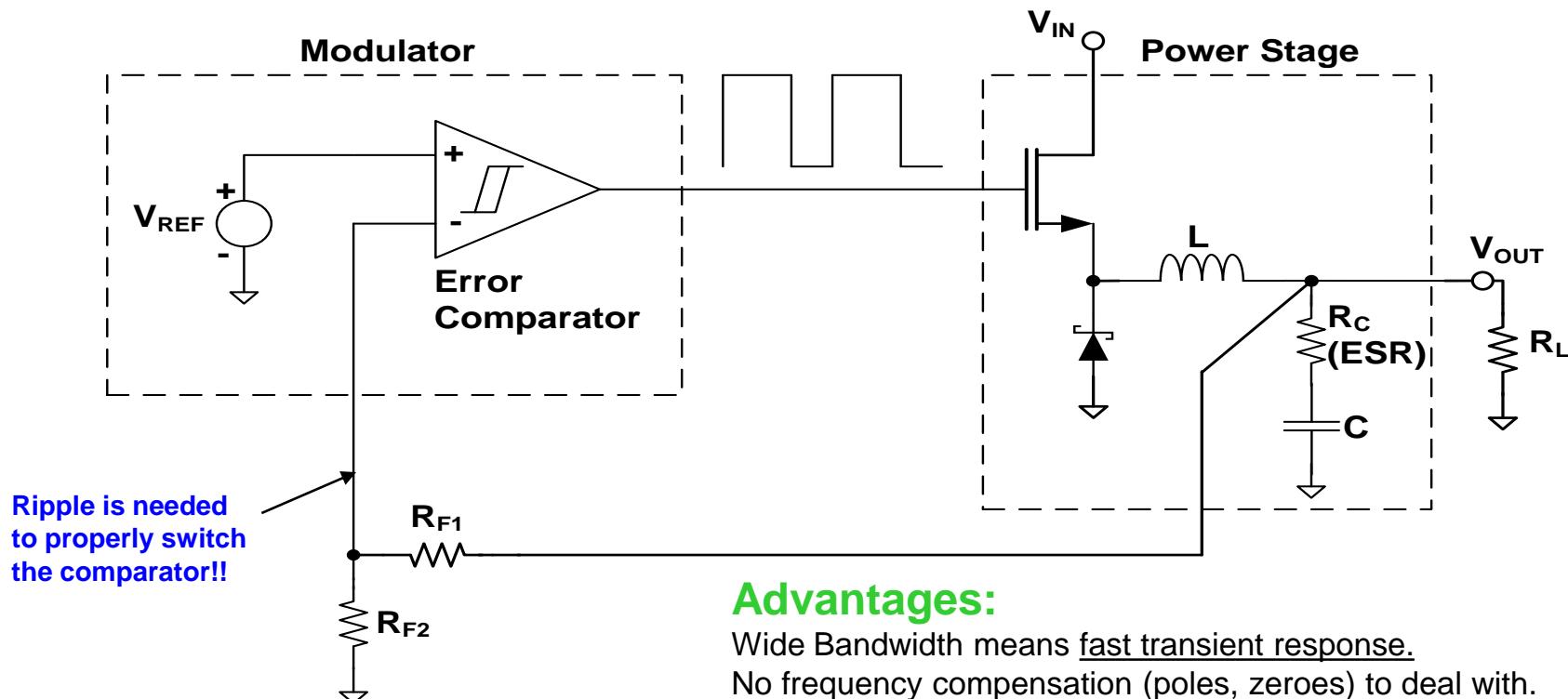
# Hysteretic Buck Regulator Basic Architecture



## Advantages:

- Wide Bandwidth means fast transient response.
- No frequency compensation (poles, zeroes) to deal with.
- $V_{IN}$  feedforward is inherent.

## Disadvantages:


$t_{ON}$  and  $t_{OFF}$ , and therefore the frequency, are functions of:  
 $V_{IN}$ ,  $V_{OUT}$ ,  $I_L$ ,  $L$ , ESR, ESL,  $V_{HYS} \cdot (R_{F1} + R_{F2}) / R_{F2}$ , and  $t_d$

→ Frequency is difficult to control!!

# **Constant-On-Time (COT) Regulation**

**Не требуется компенсация ЧХ**


# Constant On-Time – Two Methods

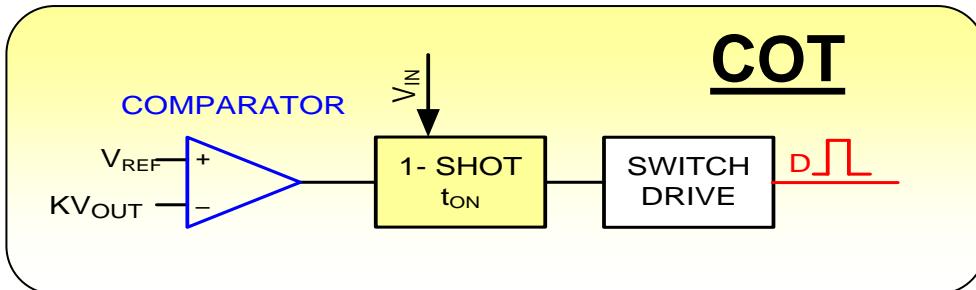
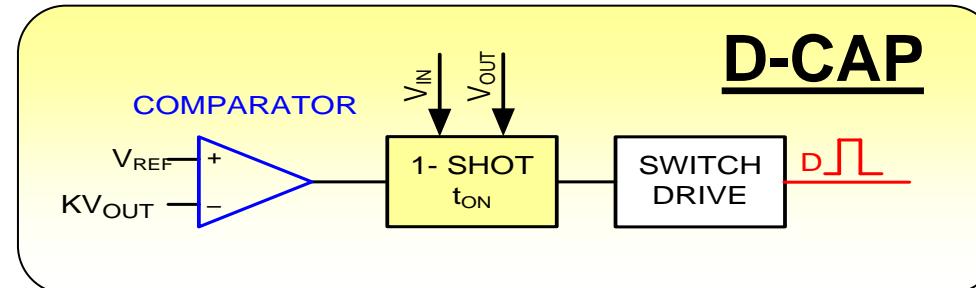
## Commonalities:

- No oscillator, but (quasi) fixed  $t_{ON}$
- Quasi-constant switching frequency
- No compensation network, no delay fastest transient response

$$t_{ON} \propto \frac{V_{OUT}}{V_{IN}}$$




## Differences:

- ON-Time also function of  $V_{OUT}$
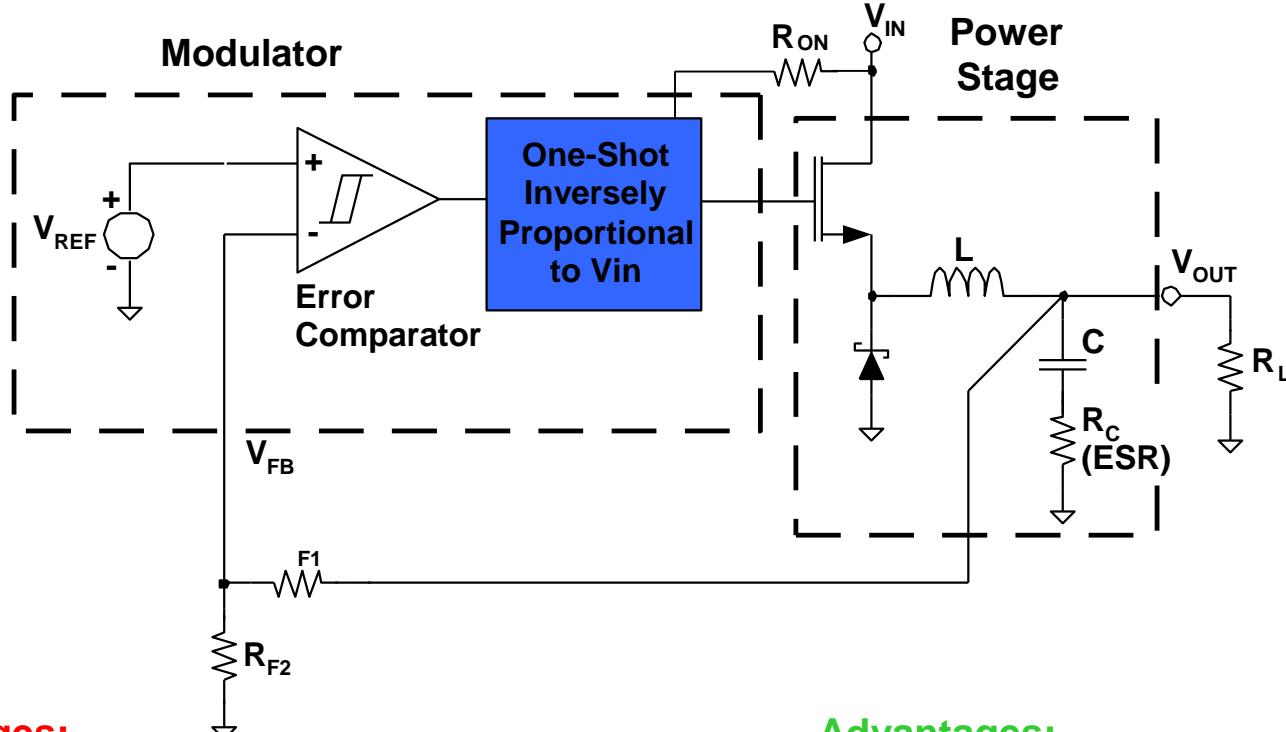
# Constant-On-time (COT) Hysteretic Regulator

The addition of a one-shot to the basic hysteretic control




## Disadvantages:

- Requires ripple at feedback comparator
- Sensitive to output noise, because it translates to feedback ripple


## Advantages:

- **Constant frequency vs.  $V_{IN}$**
- **High efficiency at light load**
- **Fast transient response for 1 cycle for fast loads**

# How does COT Regulation work?

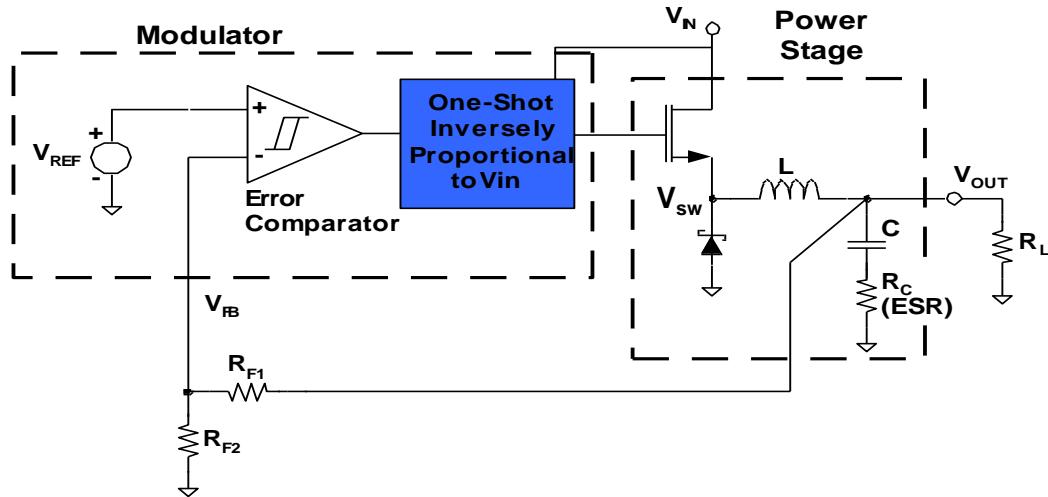


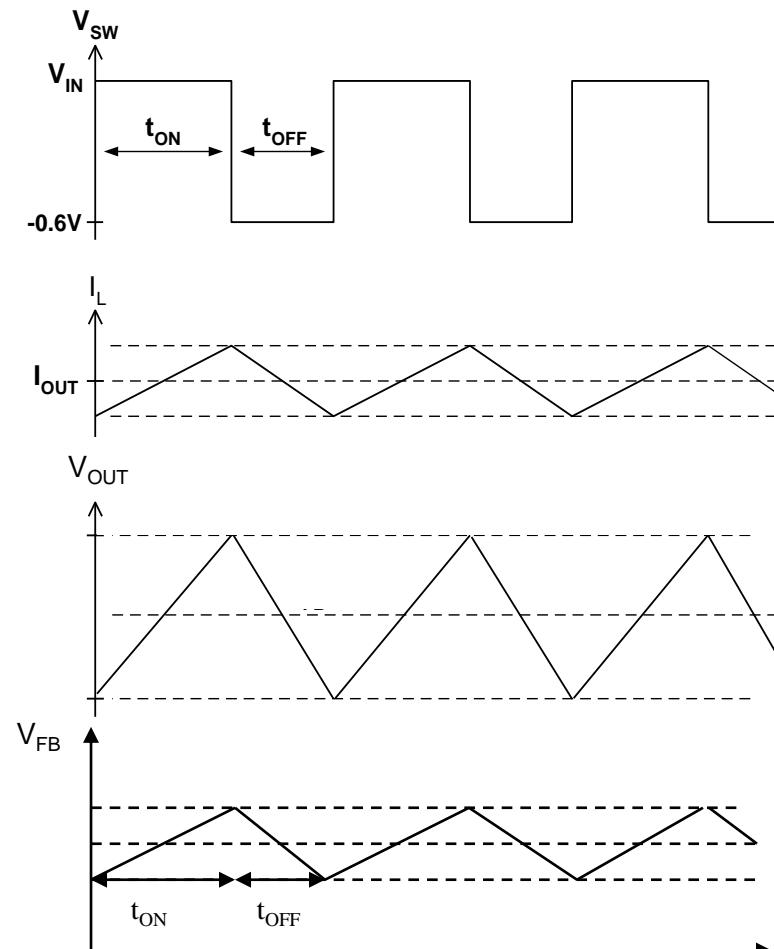- When  $V_{FB} < V_{REF}$ 
  - One-shot circuitry sets a  $t_{ON}$  time
  - $V_{sw}$  is high until  $t_{ON}$  is achieved
- Once  $t_{ON}$  is achieved
  - Switch turns off
  - Cycle starts up again when  $V_{FB} < V_{REF}$


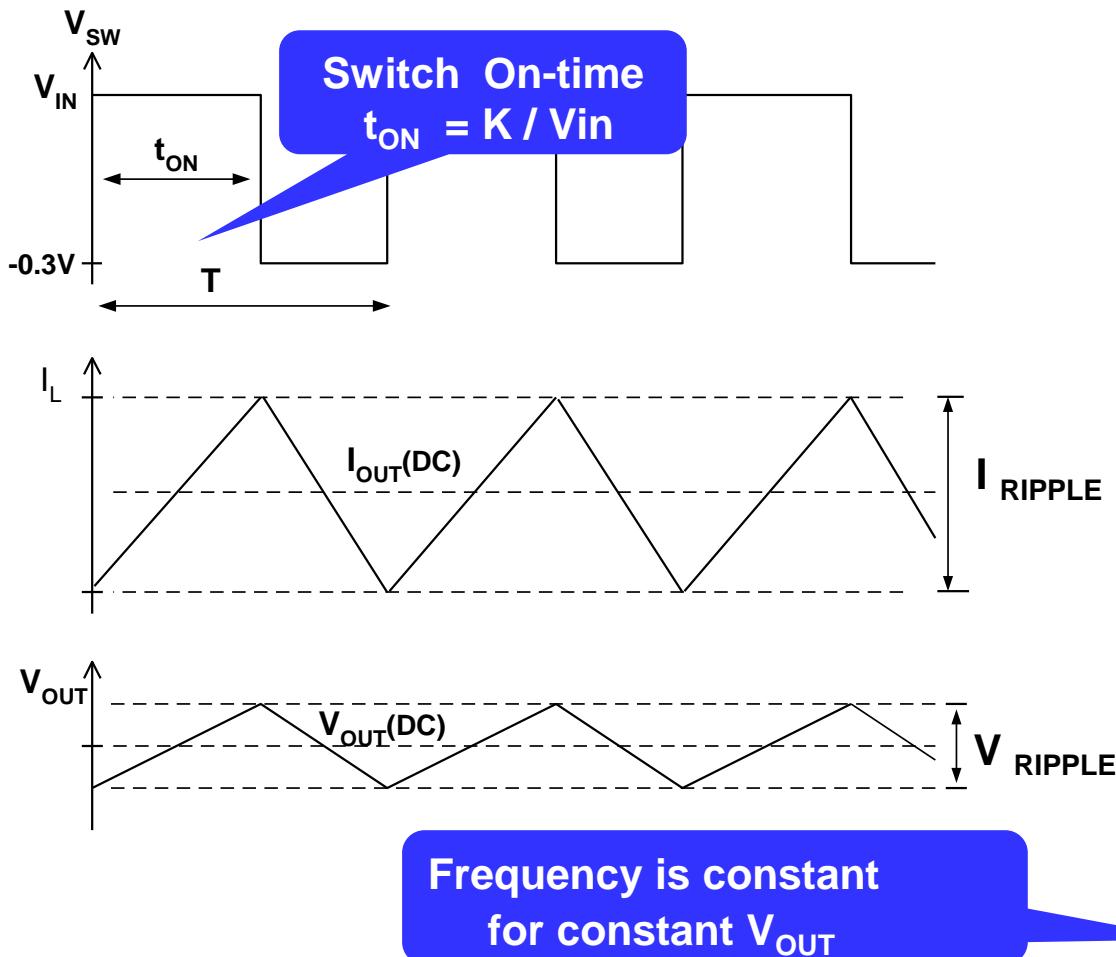
# COT Regulation with $V_{IN}$ Feedforward

Постоянная частота может быть достигнута применением прямой связи по напряжению:



**Definition of Duty Cycle:**

$$D = \frac{t_{ON}}{T} = t_{ON} \cdot f_{SW} \quad \text{EQ1}$$

**For Buck Regulator:**

$$D = \frac{V_{OUT}}{V_{IN}} \quad \text{EQ2}$$

**Setting EQ1 = EQ2:**

$$t_{ON} \cdot f_{SW} = \frac{V_{OUT}}{V_{IN}} \quad \text{EQ3}$$

**For COT with Feed-forward:**

$$t_{ON} = \frac{K \cdot R_{ON}}{V_{IN}} \quad \text{EQ4}$$

$K$  is a constant =  $1.3 \times 10^{-10}$


**Insert EQ4 in EQ3:**

$$\frac{K \cdot R_{ON}}{V_{IN}} \cdot f_{SW} = \frac{V_{OUT}}{V_{IN}}$$

**Solve for  $f_{SW}$ :**


$$f_{SW} = \frac{V_{OUT}}{K \cdot R_{ON}}$$
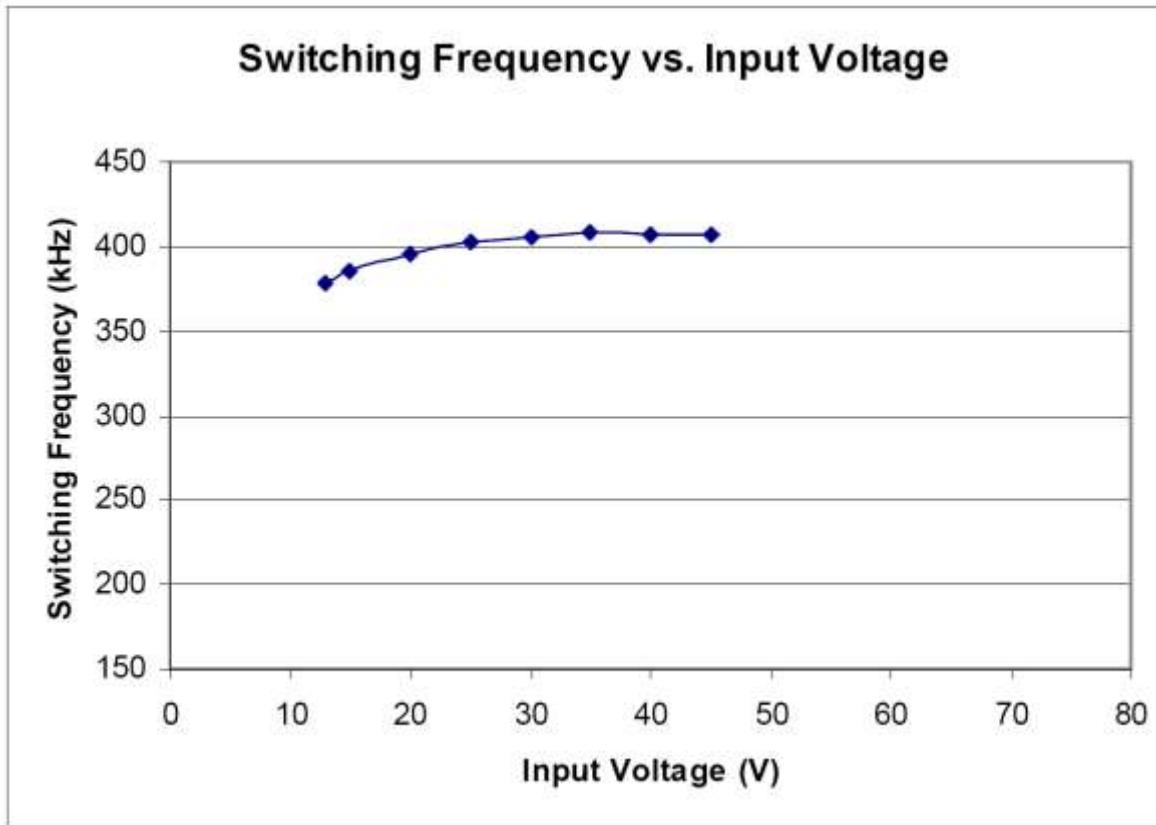
# COT Regulation with $V_{IN}$ Feedforward



Частота относительно постоянна в широком  
диапазоне входных напряжений.
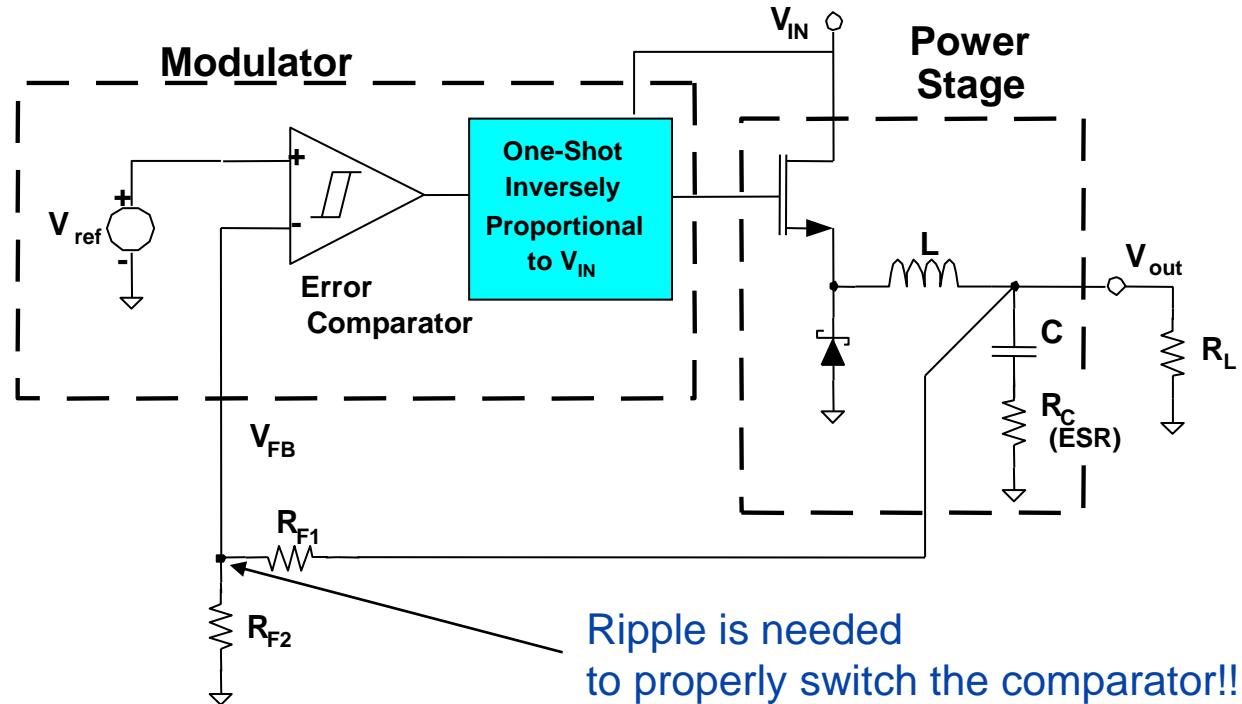
# ESR необходим для достаточных пульсаций $V_{out}$




- $T_{off}$  regulates by comparing  $V_{OUT}$  to  $V_{ref}$
- $V_{OUT}$  ripple must be large enough to overcome the comparator hysteresis
- ESR of output capacitor is directly proportional to  $V_{OUT}$  ripple
- ESR must be large enough to create sufficient  $V_{OUT}$  ripple to properly switch the comparator
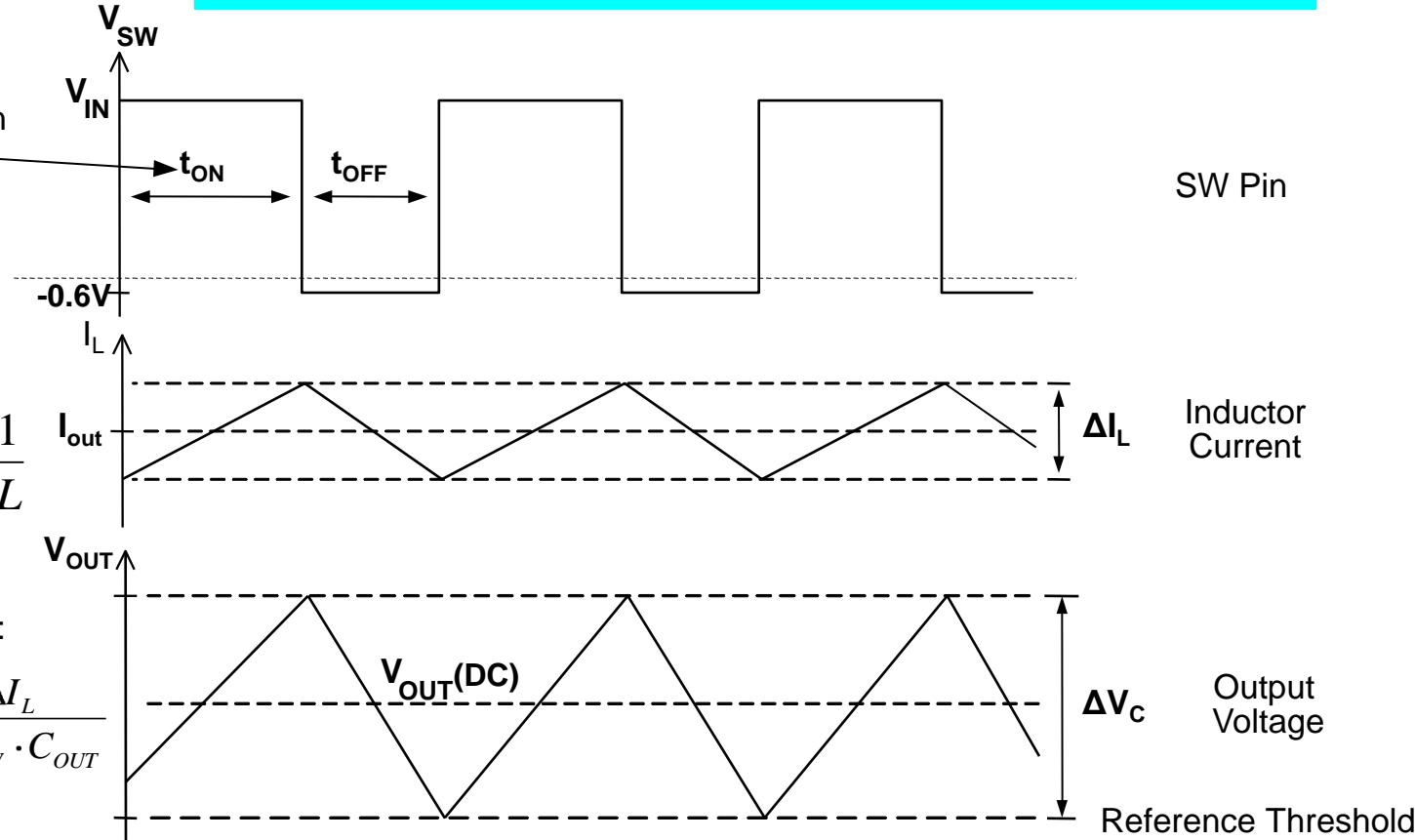
# Hysteretic Regulator Waveforms

For a given  $V_{IN}$  ON-Time is constant as load current varies

Buck Switch stays ON for an On-time determined by  $V_{IN}$  and  $R_{ON}$



Inductor's ripple current:


$$\Delta I_L = V_{in} - V_{out} \cdot t_{ON} \cdot \frac{1}{L}$$

Output voltage ripple:

$$\Delta V_{OUT} = \Delta I_L \cdot ESR + \frac{\Delta I_L}{8 \cdot f_{SW} \cdot C_{OUT}}$$


In standard COT control schemes it is recommended that a low ESR ceramic output capacitor be used in series with a resistor to provide a stable ESR
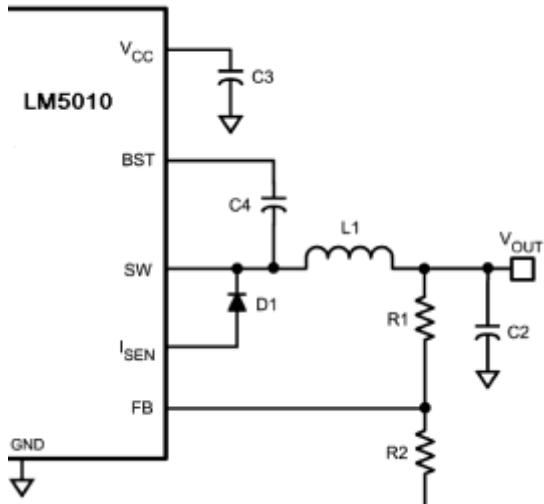
# ESR необходим для уменьшения фазового сдвига между $V_{OUT}$ и $I_{sw}$




$$V_{out} = V_{ref} \cdot \frac{R1 + R2}{R2} = V_{C2} + V_{ESR}$$

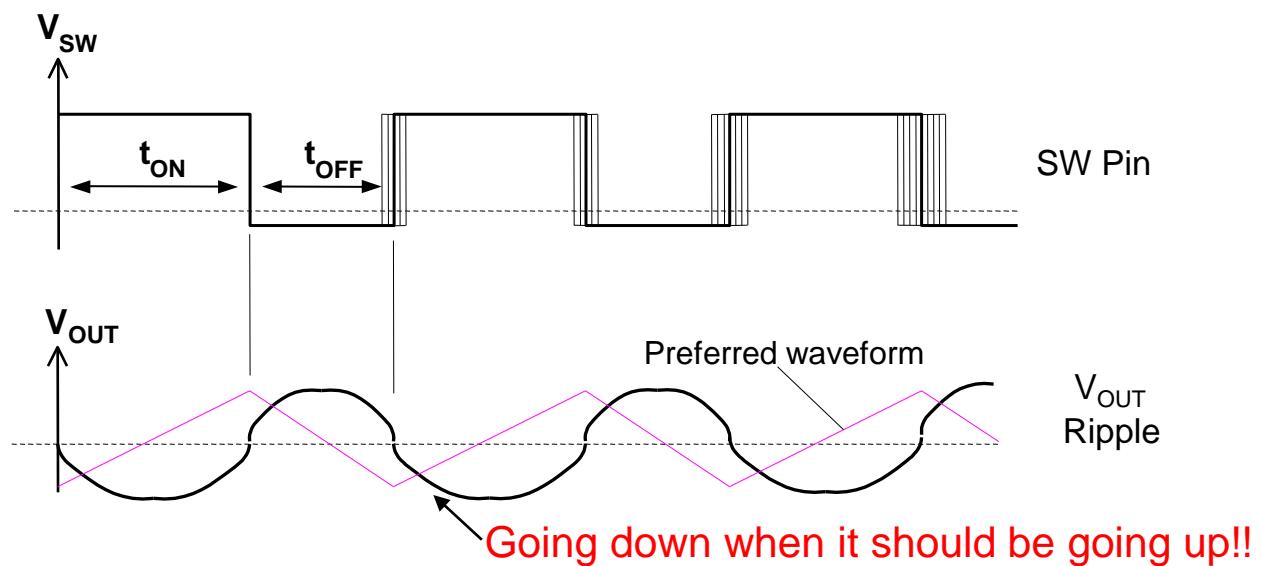- $V_{C2}$  is phase shifted 90° from inductor current waveform
- $V_{ESR}$  is in phase with inductor current waveform
- If  $V_{ESR}$  is small,  $V_{out}$  will be dominated by the phase shifted  $V_{C2}$  component causing  $V_{sw}$  to jitter and circuit to regulate poorly



# Методы добавки пульсации в ОС

Type 1  
Lowest Cost  
Configuration

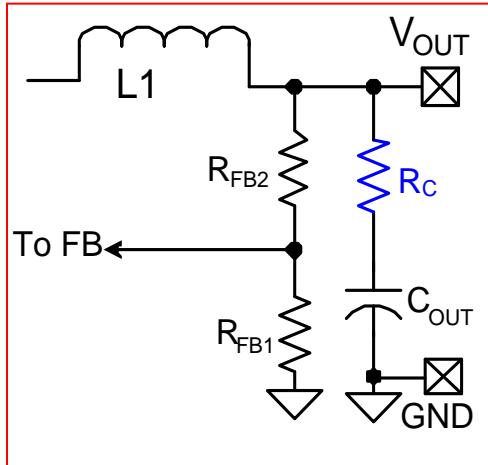


$$R_C \geq \frac{25mV}{\Delta I_{L(\min)}} \frac{V_{OUT}}{V_{REF}}$$

Controlling Output Ripple  
and Achieving ESR  
Independence in Constant  
On-Time (COT) Regulator  
Designs


National Semiconductor  
Application Note 1481  
Craig Varga  
September 2006

Type 2  
Reduced Ripple  
Configuration

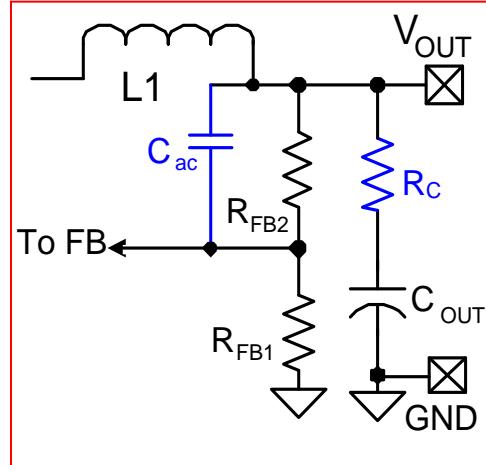

$$R_C \geq \frac{25mV}{\Delta I_{L(\min)}}$$

Type 3  
Minimum Ripple  
Configuration

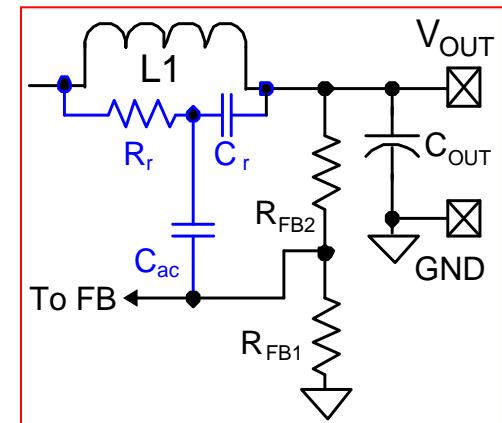



$$C_r = 3300pF$$
$$C_{ac} = 100nF$$
$$R_r \leq \frac{V_{IN(\min)} - V_{OUT}}{25mV \cdot C_r} \cdot T_{ON}$$

# LM5017/18/19

## 100V Synchronous Buck Regulator Family
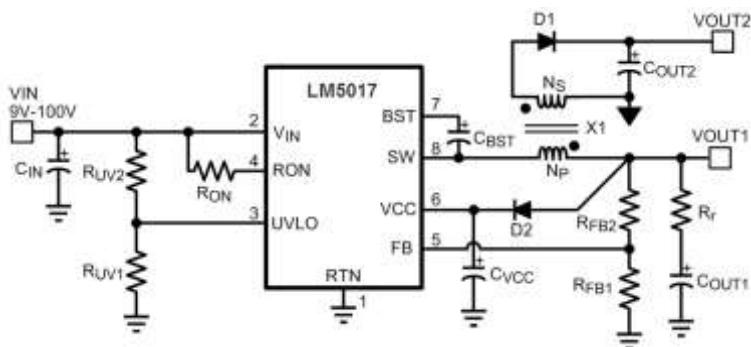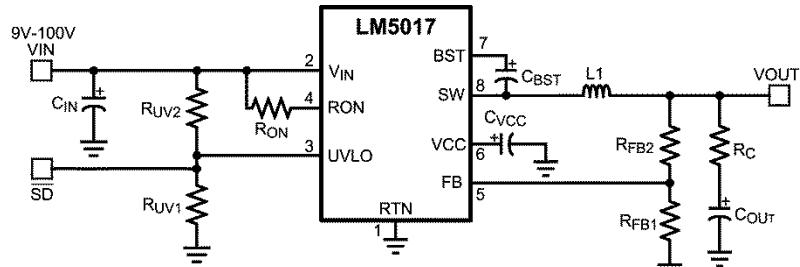
### Key Features

- Input voltage range: 9V to **100V**
- Integrated HS and LS FETs
- 600mA/300mA/100mA output current levels
- *Isolated output when used with transformer or coupled inductor*
- Integrated Input under-voltage lock-out
- **No Control Loop Compensation Required (COT)**
- **Ultra-fast transient response**
- Switching frequency adjustable to 1MHz
- Output adjustable to min 1.22V
- Precision reference,  $\pm 2.5\%$  over full temp range
- Peak current limit protection
- Thermal shutdown
- PSOP-8, LLP-8 packages
- **Available in AEC-Q100 Grade 1  
( $T_{jmax}=125^\circ\text{C}$ )**



### Availability / Pricing


Order Code	Load Current [mA]	1K Web Price
LM5017	600	\$1.65
LM5018	300	\$1.40
LM5019	100	\$1.25

# **D-CAP**

**Не требуется компенсация ЧХ  
(эквивалент СОТ)**
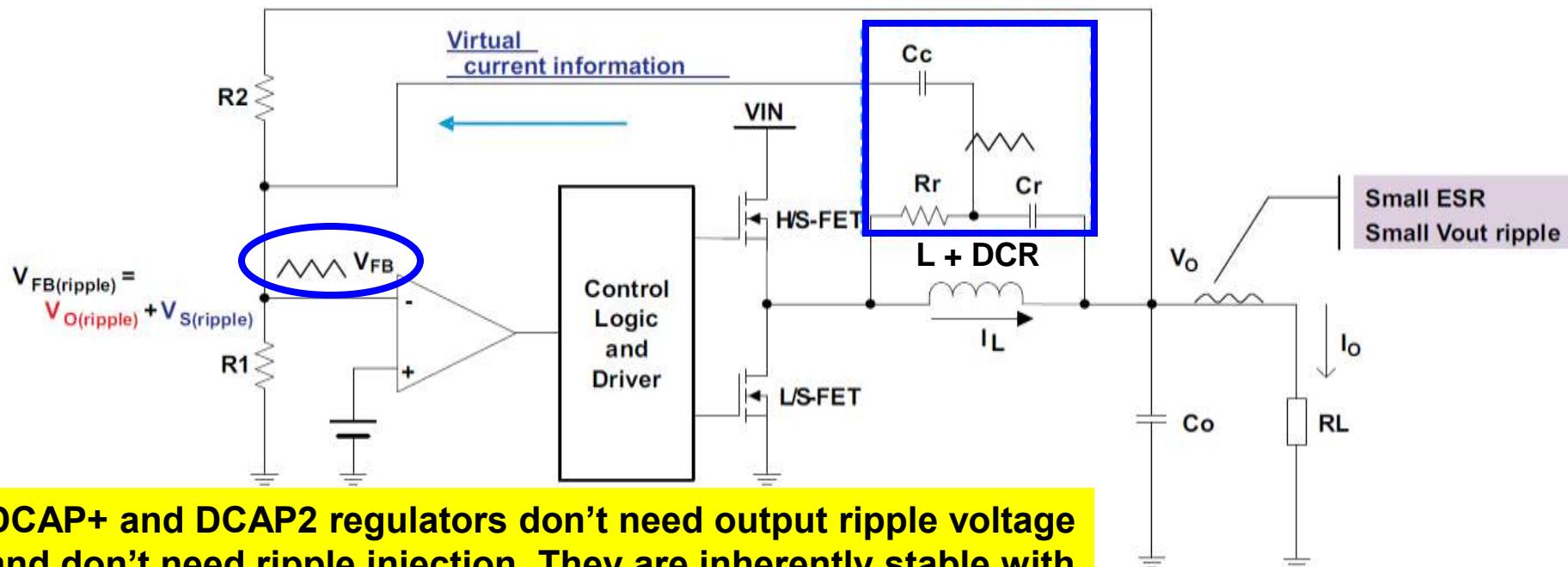
# D-CAP Mode - Ripple Injection Networks allows Multilayer Ceramic Capacitors (MLCC)

- D-CAP regulators need 10 ... 15mV peak-to-peak voltage ripple on feedback-pin
- Ripple comes usually from output voltage ripple (caused by certain ESR of  $C_o$ )
- Output Voltage Ripple can be avoided by use of Ripple Injection Network
- App note: “D-CAP™ Mode With All-Ceramic Output Capacitor Application” [SLVA453](#)
- Ripple Injection Network generates 10 ... 15mV VFB ripple w/o any ripple on  $V_{OUT}$ : Enables use of MLCC




DCAP+ and DCAP2 regulators don't need output ripple voltage and don't need ripple injection. They are inherently stable with ceramic output capacitors (MLCC)

# D-CAP Mode – Mid V<sub>IN</sub> Converter Portfolio

Device	I <sub>OUT</sub>	Power Path		Bias V <sub>IN</sub> (V)		typ RDS <sub>on</sub> (mΩ)		V <sub>OUT</sub> (V)			Package	Size (mm x mm)
		(A)	min	max	min	max	HS	LS	min	max	Tol. (%)	
<a href="#">TPS53314</a>	6	3	15	4.5	25	20	7.5	0.6	5.5	1	QFN40	5 x 7
<a href="#">TPS53318</a>	8	3	21	4.5	21	9	5	0.6	5.5	1	QFN22	5 x 6
<a href="#">TPS51315</a>	10	3	14	4.5	5.5	19	7	0.7 5	5.5	1.6	QFN40	5 x 7
<a href="#">TPS53319</a>	12	3	21	4.5	21	9	5	0.6	5.5	1	QFN22	5 x 6
<a href="#">TPS53315</a>	12	3	15	4.5	25	19	7	0.6	5.5	1	QFN40	5 x 7
<a href="#">TPS53353</a>	20	3	15	4.5	25	5.5	2.2	0.6	5.5	1	QFN22	5 x 6
<a href="#">TPS53355</a>	30	3	15	4.5	25	5	2	0.6	5.5	1	QFN22	5 x 6



All devices with single grounded PowerPAD for reduced EMI
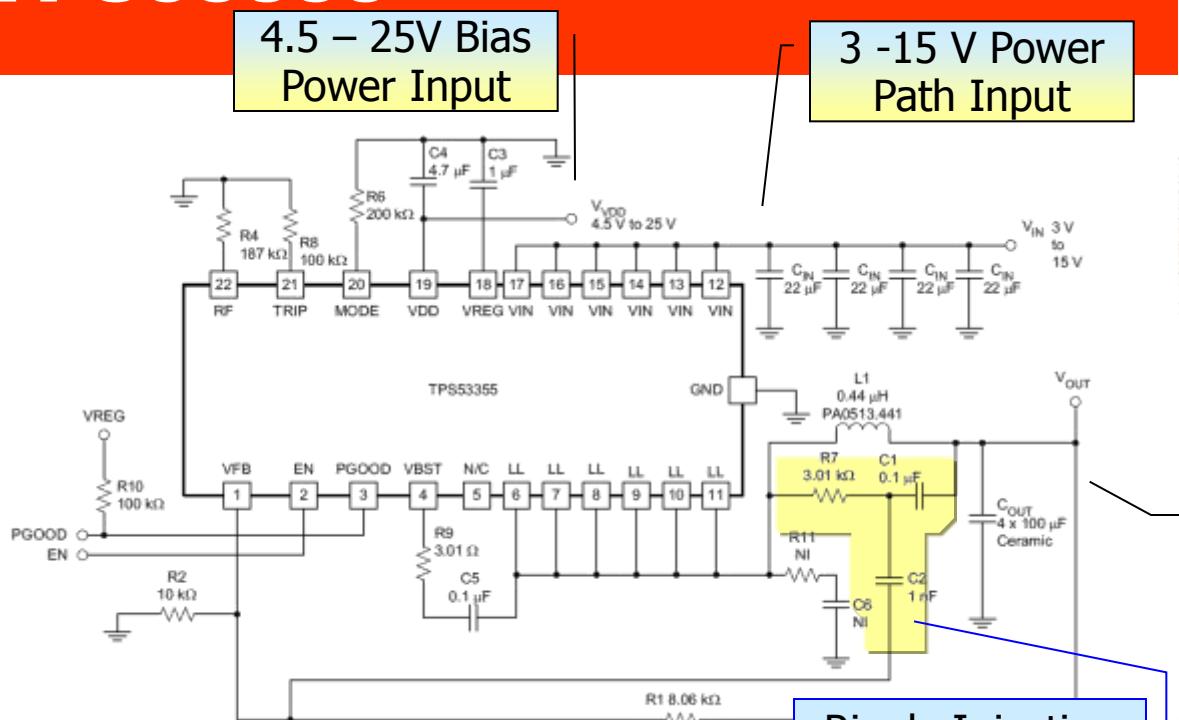
# 30A 3-15VIN D-CAP™ SR Buck Converter w/ ECO-Mode™ TPS53355



- Fast Transient D-CAP™ Mode
- No Loop Comp. Required
- Select. FCCM / ECO-(Skip)- Mode
- Pre- Bias Start- up
- Output OV / UV Protect. & Power Good
- Programmable Current Limit
- 8 selectable switching freq., 4 selectable SS times
- 5V LDO Output (30mA)

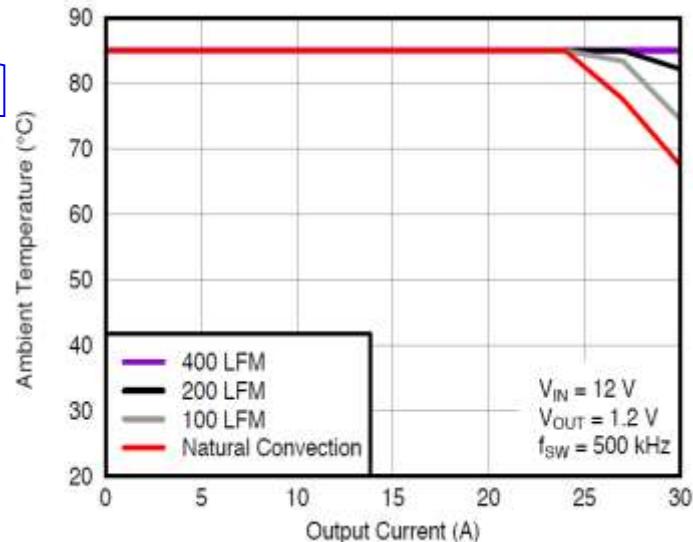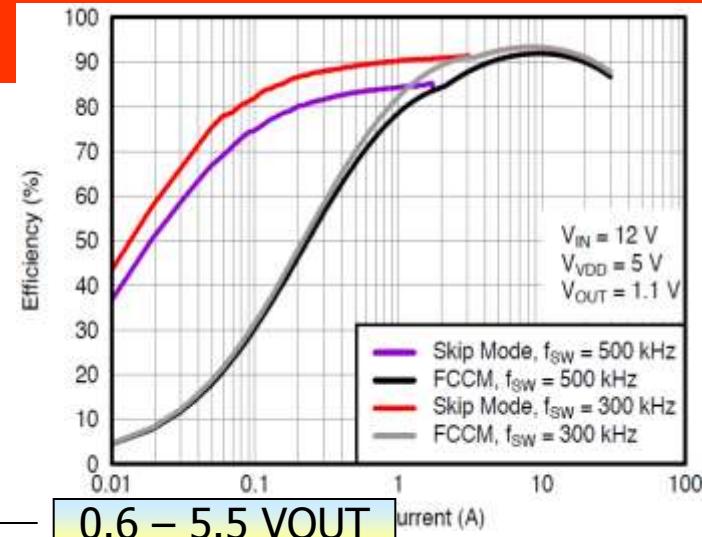
Ripple Injection Network  
Enables Use of  
MLCC Output Caps



# **Constant-On-Time (COT) Regulation with Emulated Ripple Mode (ERM)**

**Малые пульсации выходного напряжения  
Меньше компонентов**


# Improved Constant On-Time: COT-ERM

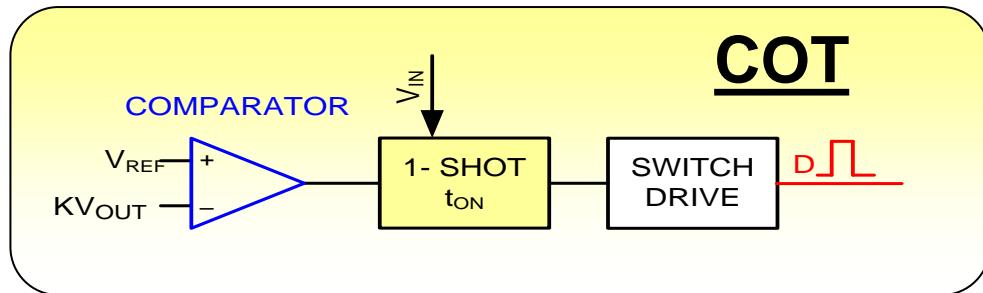
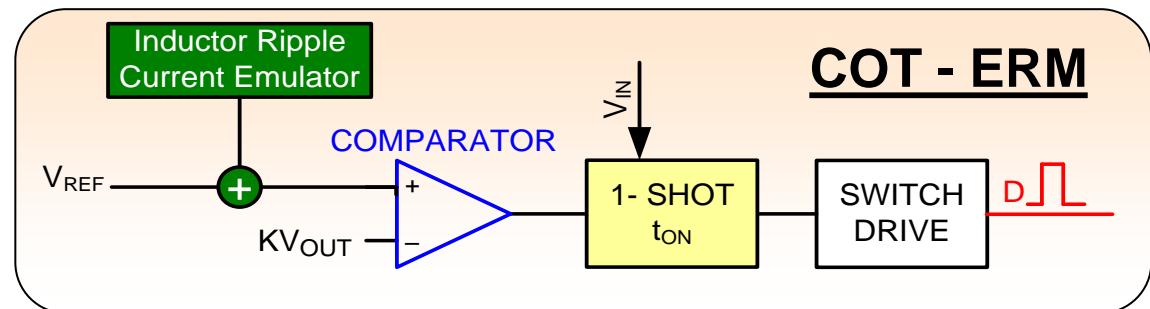
## Commonalities:

- No oscillator, but (quasi) fixed t<sub>ON</sub>
- Quasi-constant switching frequency
- No compensation network, no delay fastest transient response

$$t_{ON} \propto \frac{V_{OUT}}{V_{IN}}$$




## Differences:

**Need for output voltage ripple:**

- **COT: ~10 – 15mV ripple needed on feedback-pin**; can reduced to **0mV with ripple injection circuit**
- **COT- ERM No output ripple needed**, internally **emulated**

# Как эмулируют пульсации?

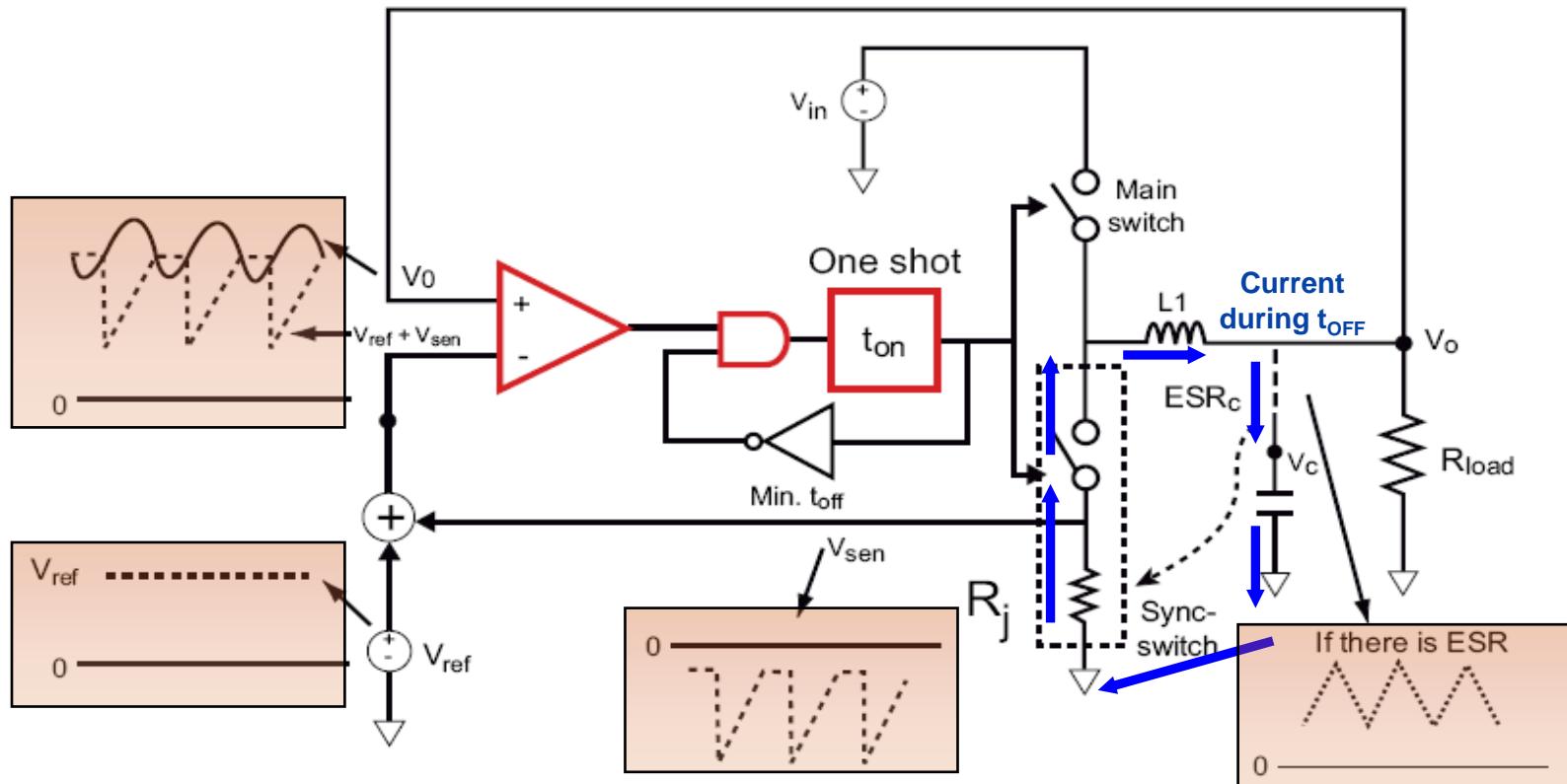

- ESR current can be sensed through  $R_j$  ( $R_{DS\_ON}$  of the Low Side Mosfet)
- The inverted  $V_{SEN}$  is the replication of  $V_{ESR}$  ripple during  $t_{OFF}$
- This is added to the DC reference voltage  $V_{ref}$  before comparing to  $V_{OUT}$
- No ESR is required on the output capacitor

# **SIMPLE SWITCHER®**


## **Regulators**

### **LM310x Family**

# LM310x Synchronous SIMPLE SWITCHER® Family
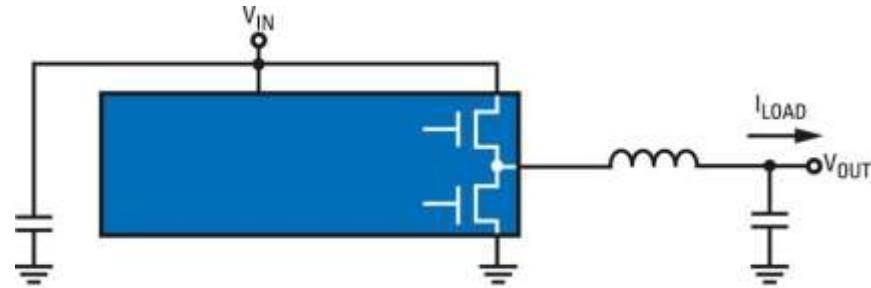
## Key Features

- Vin Range **4.5V to 42V** (0.75A, 2.5A)
- **Constant ON-Time with Emulated Ripple Mode**
- Fast transient response
- No external compensation required
- Adjustable Output Voltage (**0.8V**-25V)
- 1.5% Initial Accuracy at 25°C
- **Precision Enable**
- Adjustable Frequency (50kHz-1MHz)
- Adjustable Soft-Start
- Stable with Ceramic Capacitors
- Packages
  - eTSSOP-16 (0.75A)
  - eTSSOP-20 (1.5A, 2.5A)
  - micro SMD (1A)




## Availability / Pricing

Order Code	Load Current [A]	Vin [V]	1K Web Price
LM3103	0.75	42	\$1.80
LM3100	1.5	36	\$2.35
LM3102	2.5	42	\$2.59

# **D-CAP2**

**Малые пульсации выходного напряжения  
(эквивалент СОТ-ЕРМ)**


# Improved Constant On-Time: D-CAP2

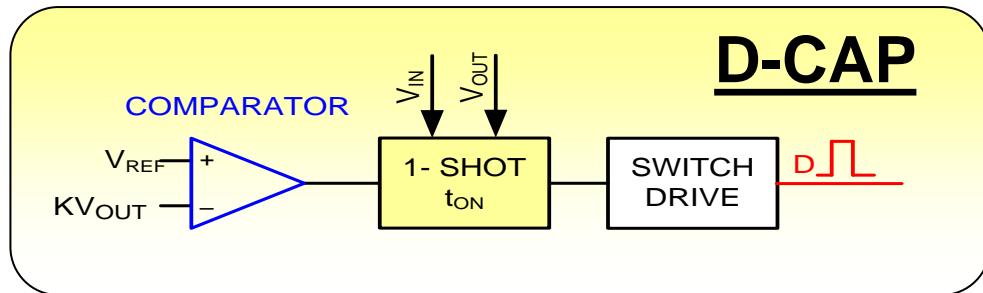
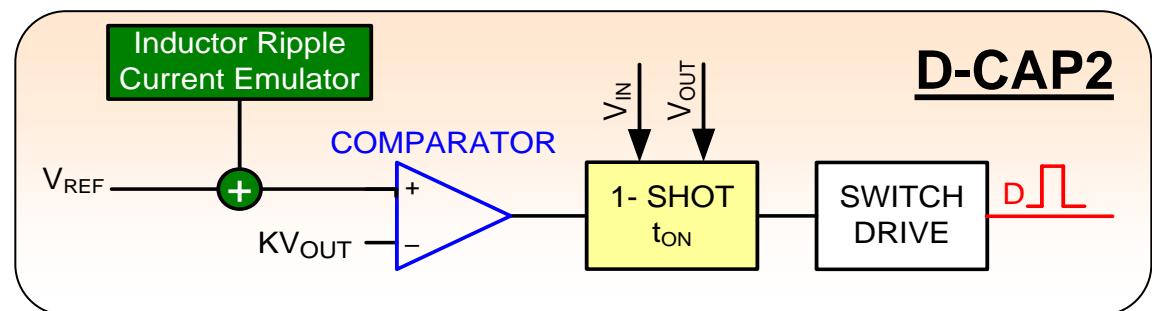
## Commonalities:

- No oscillator, but (quasi) fixed  $t_{ON}$
- Quasi-constant switching frequency
- No compensation network, no delay fastest transient response

$$t_{ON} \propto \frac{V_{OUT}}{V_{IN}}$$




## Differences:

Need for output voltage ripple:


- D-CAP: ~10 – 15mV ripple needed on feedback-pin; can reduced to 0mV with ripple injection circuit
- D-CAP2: No output ripple needed, internally emulated

# D-CAP2 mode feature

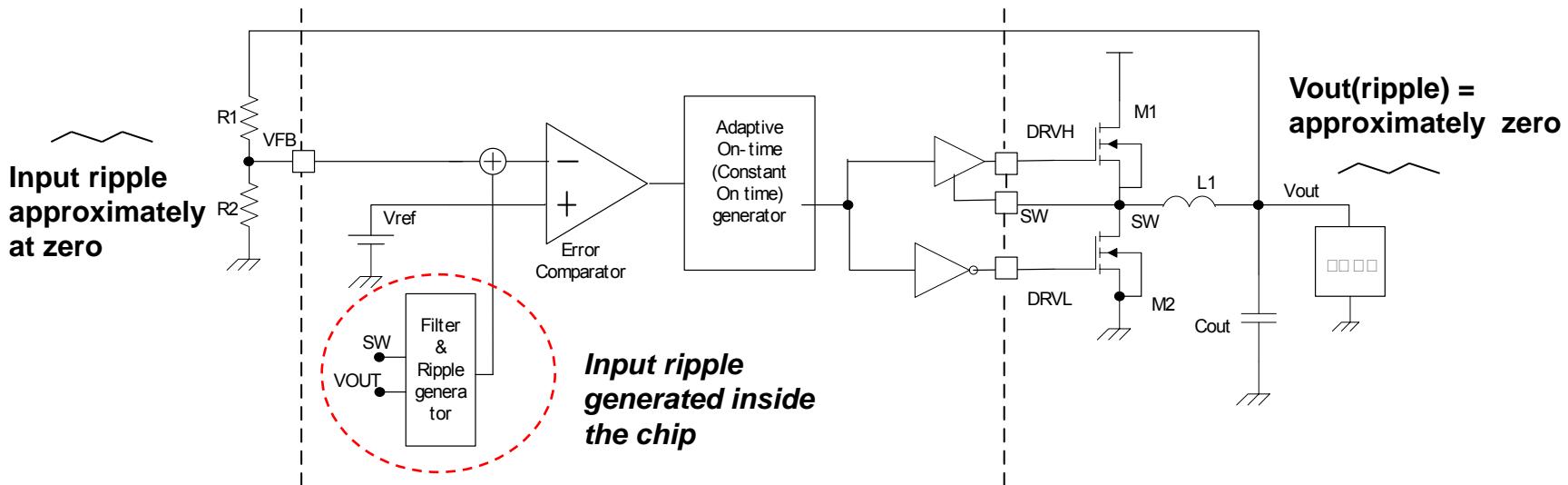

- (1) TI D-CAP2 mode topology is next generation DCAP mode which integrates a switching injection circuit to allow use of ceramic output capacitors.
- (2) DCAP2 mode is stable even if the Vout ripple voltage is zero. This allows the use of ceramic output capacitors.
- (3) DCAP2 mode has identical operation as DCAP mode.
- (4) Input feedback voltage (Vfb) to error comparator directly without an error amplifier

# D-CAP2 Converters Portfolio

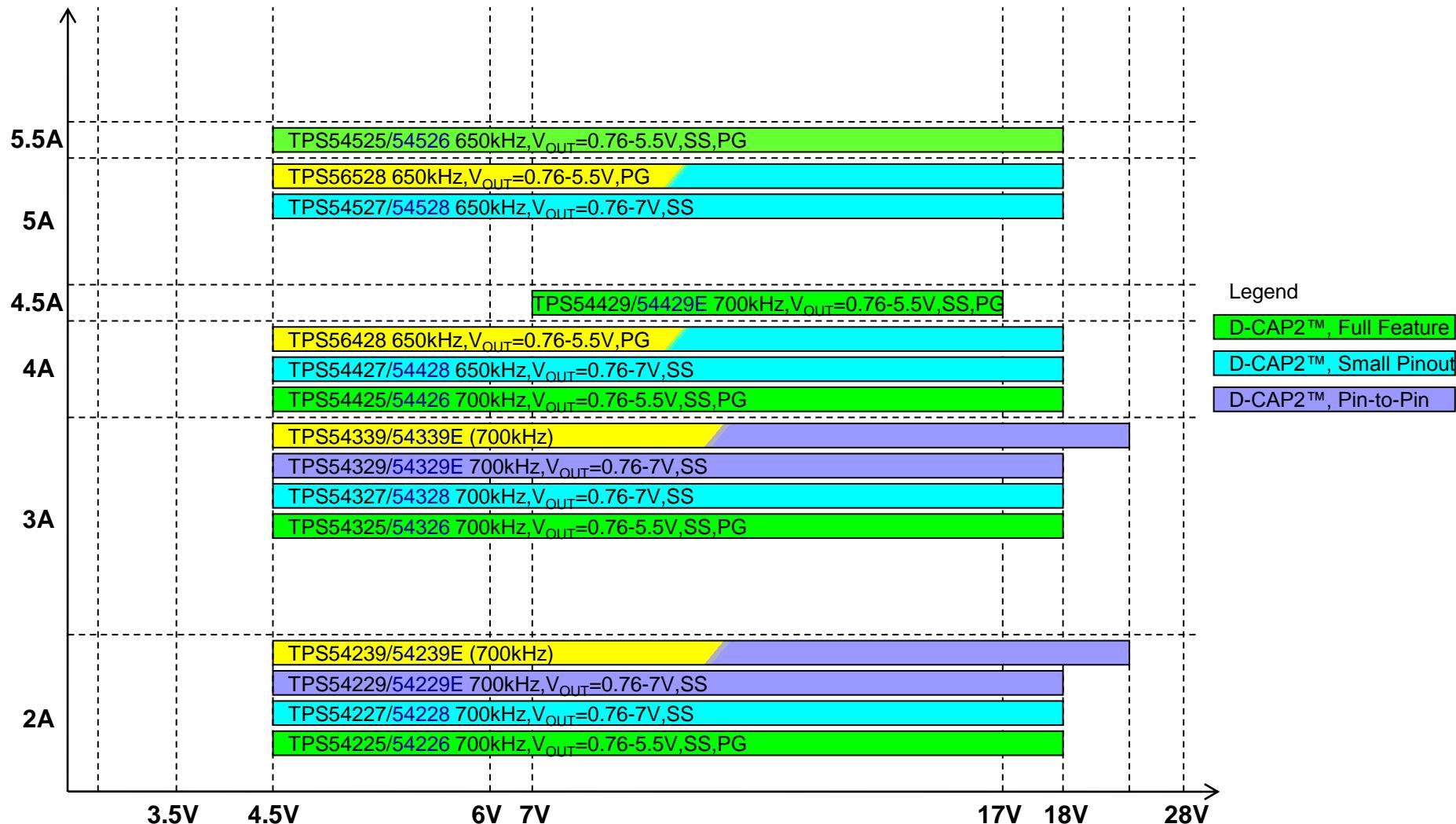

# Mid VIN SR Buck D-CAP2 Converters TPS54x27 / x28 (aka Kirishima)

## ОСОБЕННОСТИ


- Fast Adaptive On-Time (D-CAP2) Control Architecture
- Very Low Resistance MOSFETs
- Fixed 700kHz Switching Frequency
- Adjustable Soft-Start Time
- Auto-Skipping Eco-mode: TPS54x28

## ПРЕИМУЩЕСТВА

- High Performance with 2 x 22uF Ceramic Cout
  - Faster than 20us transient response time
  - Less 10mVp-p output voltage ripple
  - No compensation components needed
- 90% Efficiency; Optimized for Low Vout
- 1,5 uHn Small Inductor
- Reduces Inrush Currents During Startup
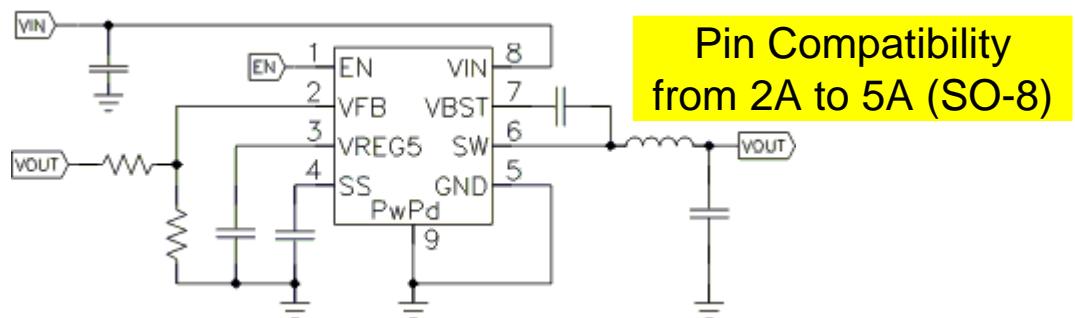
## ПРИМЕНЕНИЯ

- Digital TV
- Industrial
- Networking Home Terminal
- Digital Set Top Box



Eco-mode →	TPS54227	2	-	4.5-18	700k	0.76-7	DDA
	TPS54228	2	-	4.5-18	700k	0.76-7	D,DDA,DRC

# **Advanced COT Control Methods**


**Быстрые  
Малые пульсации выходного напряжения**

# Constant On-Time Control Modes
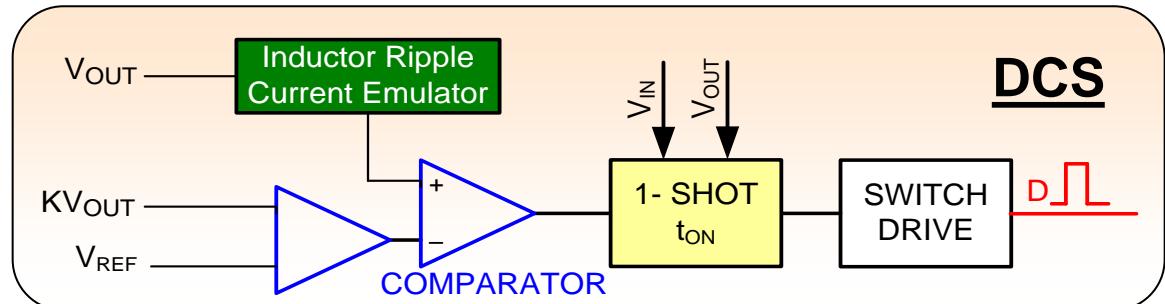
## Commonalities:

- No oscillator, but (quasi) fixed tON
- Quasi-constant switching frequency
- No compensation network, no delay
- Fastest transient response

$$t_{ON} \propto \frac{V_{OUT}}{V_{IN}}$$




Direct Control with Seamless Transition to Power Save Mode

## Differences:
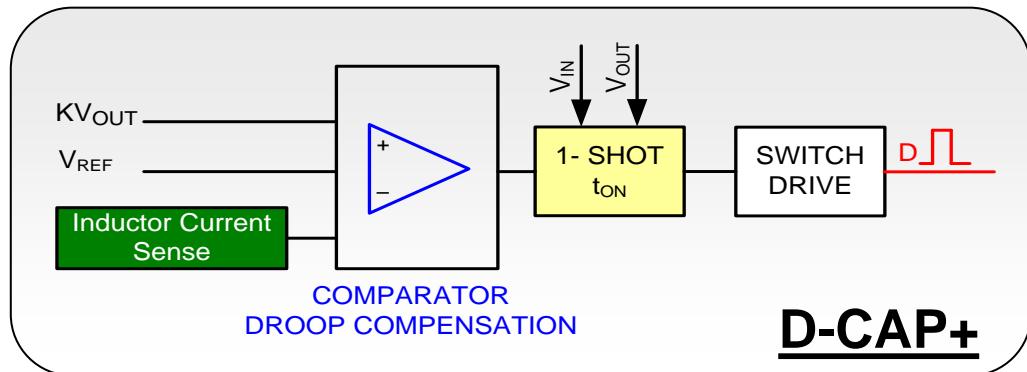
### Need for output voltage ripple:

- **DCS:** **No output ripple needed**, inductor-/ switch-**current ripple used**; is basically combination of D-CAP and VM
- **D-CAP+:** **No output ripple needed**, inductor-/ switch-**current ripple used**; is basically combination of D-CAP and CM



D-CAP+

# **Advanced COT DCS**

**Direct Control with Seamless Transition  
to Power Save Mode**

# Преимущества СОТ DCS архитектуры

- 100% Duty-Cycle Mode
- Быстрый отклик
- Отличная стабилизация по нагрузке
- Высокий КПД во всех режимах
- Мягкая работа в пограничном режиме номинал/ХХ
- Фиксированная частота в стабильном режиме
- Отсутствие компенсации ЧХ
- Малый размер компонентов

# TPS6213x/4x/5x COT DCS

## 3...17V V<sub>IN</sub>, 1-3A, 3MHz Step-Down Converters in 3x3mm QFN

### Features


- High Efficiency Step Down Converter with DCS-Control™
- VIN range from 3 to 17V
- Adjustable V<sub>OUT</sub> from 0.9 to 6.0V
- Fixed V<sub>OUT</sub> options: 1.8V, 3.3V, 5.0V
- Output current up to: 3A (TPS62130)  
2A (TPS62140)  
1A (TPS62150)
- Seamless transition to Power Save Mode
- Pin-selectable switching frequency (full, half)
- 100% Duty Cycle Mode
- Programmable Soft Start and Tracking
- Quiescent current of 17µA (typ.)
- Power Good

### Applications

- Solid State Disk Drives
- Embedded and mobile Computing
- Industrial applications
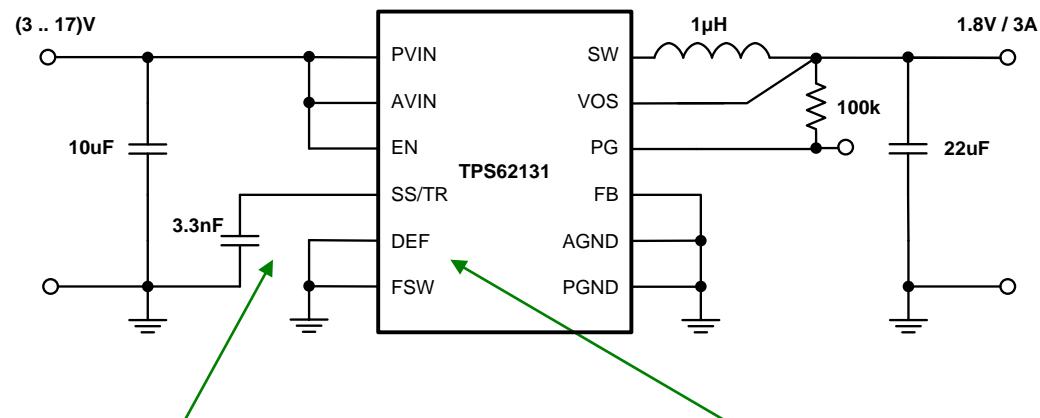
### Benefits

- High VIN converter with small solution size
- 12V → 3.3V / 3A utilizing a 1uH inductor
- DCS-Control™ regulation is fast and accurate
- Low quiescent current and selectable switching frequency for high efficiency
- VFB control allows for constant current source applications



Cstart	Adjustable Startup
TR	FB Voltage Control

DEF	Pin Selectable Output Voltage
FSW	Pin Selectable Switching Frequency

# DCS-Control™ Devices

TPS62230  
(Vin=6V with 500mA)

TPS62130/40/50  
(Vin= 17V with 3A/2A/1A)


TPS62160/70  
(Vin=17V with1A/0.5A)

TPS62080  
(Vin=6V with 1.2A)

TPS62090  
(Vin=6V with 3A)

TPS62125 (2Q12)

**TPS62130**

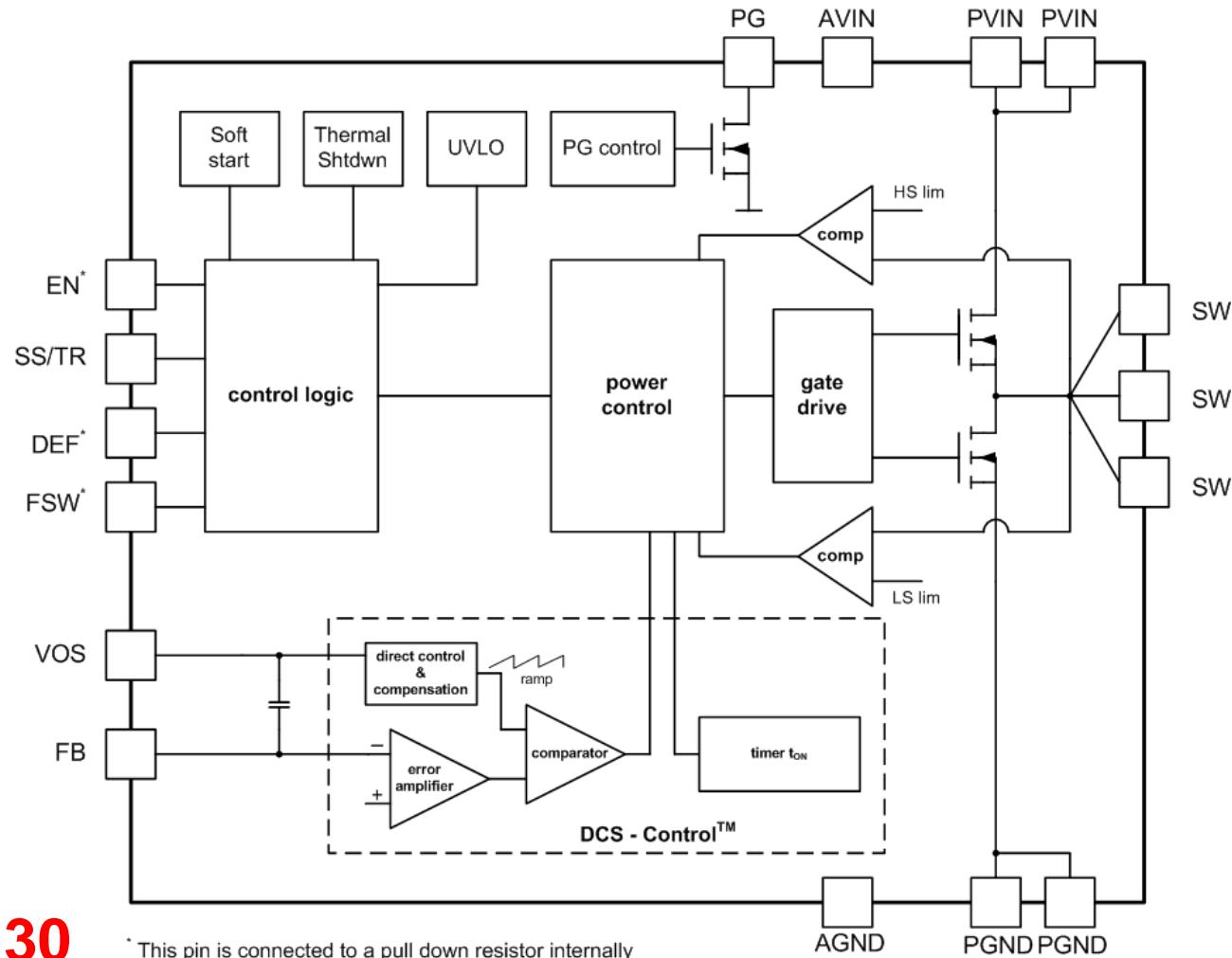


\* This pin is connected to a pull down resistor internally  
(see Detailed Description section).

# **Constant Frequency**

**Традиционны  
Оптимальны для подавления помех**

# Constant Frequency Control Modes


## Voltage Mode

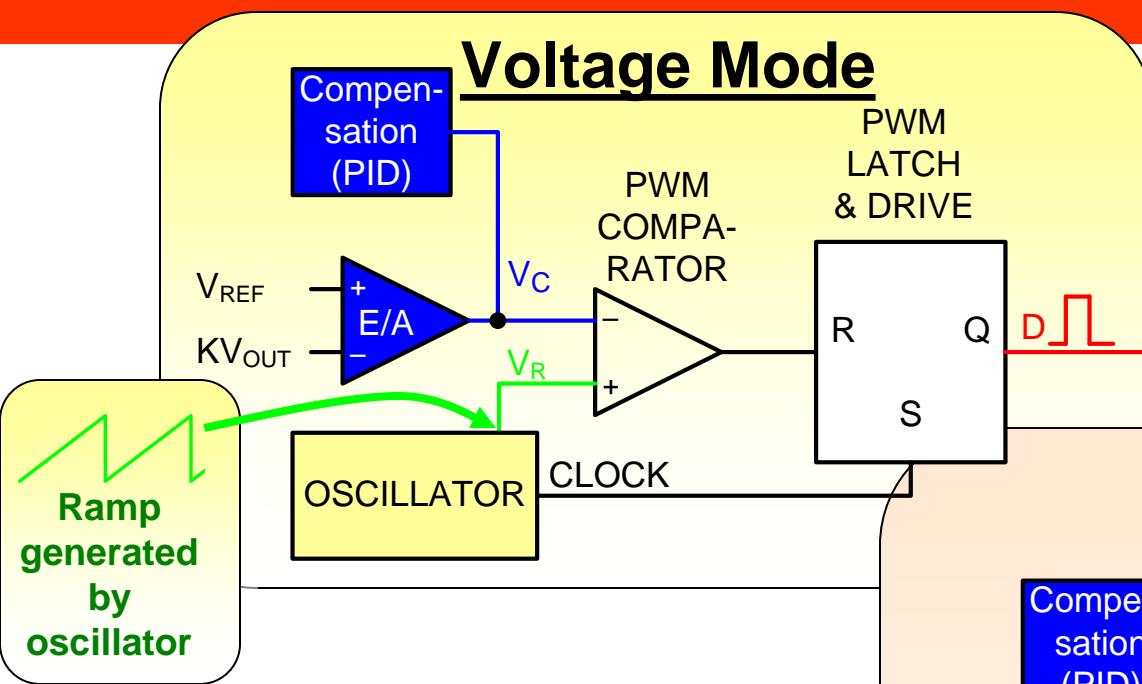

### Commonalities:

- Internal clock oscillator
- Error Amplifier amplifies difference b/w  $V_{REF}$  and  $V_{SENSE}$
- Compensation Network stabilizes control loop but introduces also delays

## (Peak) Current Mode

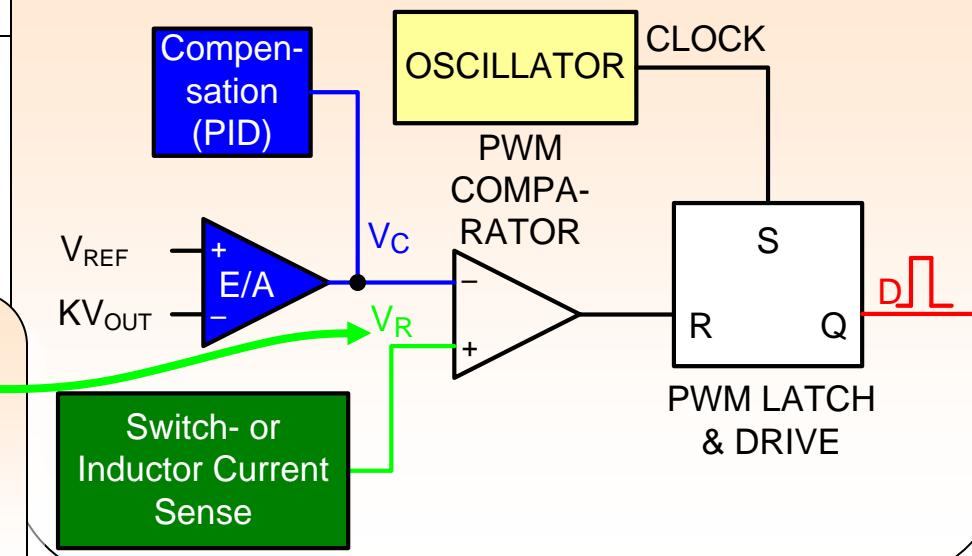

### Differences:


- Method for generating the "Ramp"
  - Oscillator
  - Current Sense

Ramp generated by switch- or inductor-current sensing

# **Voltage Mode**

**Простые синхронизируемые**

# Basic Voltage Mode PWM DC-DC Converter

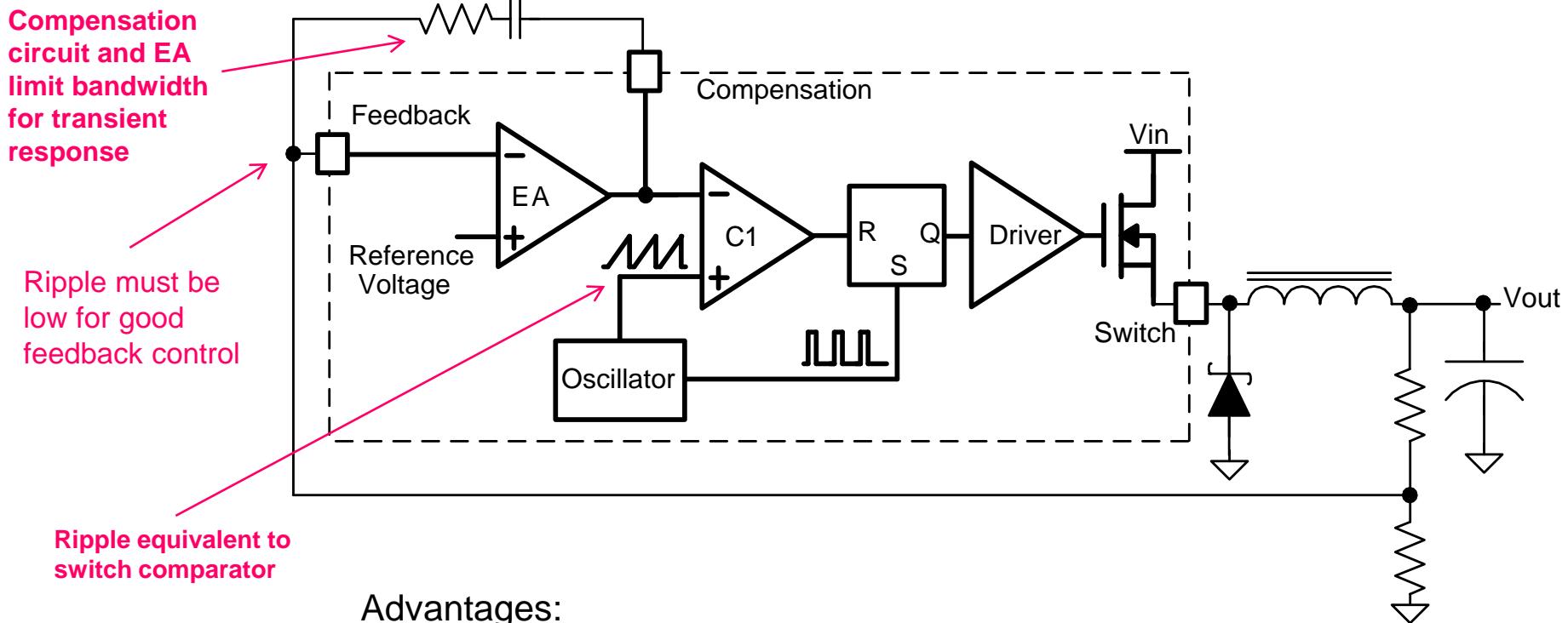

## Advantages:

Fixed frequency, low ripple (necessary)

## Disadvantages:

Fixed frequency, limited bandwidth → slower transient response vs. COT

# **SIMPLE SWITCHER®** **Regulators**


## **LM2267x Family**

**Ease of Use Regulators**

# LM2267x SIMPLE SWITCHER® Family
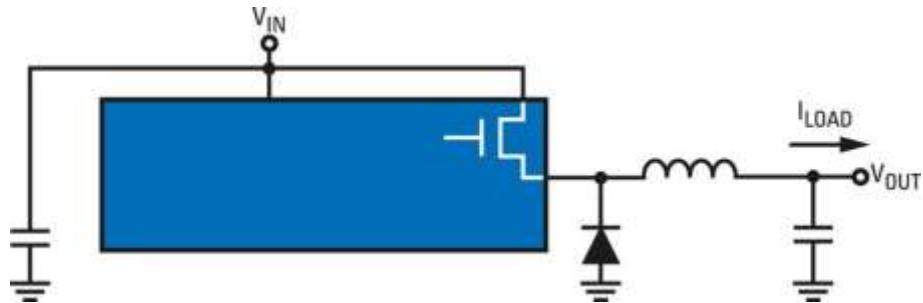
## Key Features

- Vin Range **4.5V** to **42V**
- Current Outputs: 0.5A, 1.0A, 2.0A, 3.0A, 5.0A
- Internally compensated ***V<sub>in</sub>* feed forward voltage mode control**
- Output Voltages options:
  - Adjustable range (1.285V-30V)
  - Fixed: 5.0V
- **1.5% Initial Accuracy at 25°C**
- 2.0%  $V_{OUT}$  Accuracy over Line, and Full Temperature ( $T_j = -40^\circ C$  to  $+125^\circ C$ )
- **Precision Enable**
- Optional fixed Operating Frequency: 500kHz
- **Adjustable Frequency (200kHz-1MHz)**
- **Frequency Sync (500kHz – 1MHz)**
- Adjustable Current Limit
- External Soft-Start
- Stable with Ceramic Capacitors
- **Available in AEC-Q100 Grade 1 ( $T_{jmax} = 125^\circ C$ )**
- Packages: TO-263-7 THIN, PSOP-8




## Availability / Pricing

Order Code	Iout (A)	Adj Cur Limit	Soft Start	Enable	Fsync / Fadj	1k Web Price
LM22674	0.5					\$1.32
LM22671	0.5		✓	✓	✓	\$1.38
LM22675	1.0			✓		\$1.68
LM22672	1.0		✓	✓	✓	\$1.78
LM22680	2.0		✓	✓	✓	\$1.85
LM22670	3.0			✓	✓	\$1.98
LM22673	3.0	✓	✓			\$1.98
LM22676	3.0			✓		\$1.92
LM22677	5.0			✓	✓	\$3.38
LM22678	5.0				✓	\$3.25
LM22679	5.0	✓	✓			\$3.38

# **Current Mode Regulation**

**Синхронизируемые  
Простые в компенсации  
Простые в объединении по току**
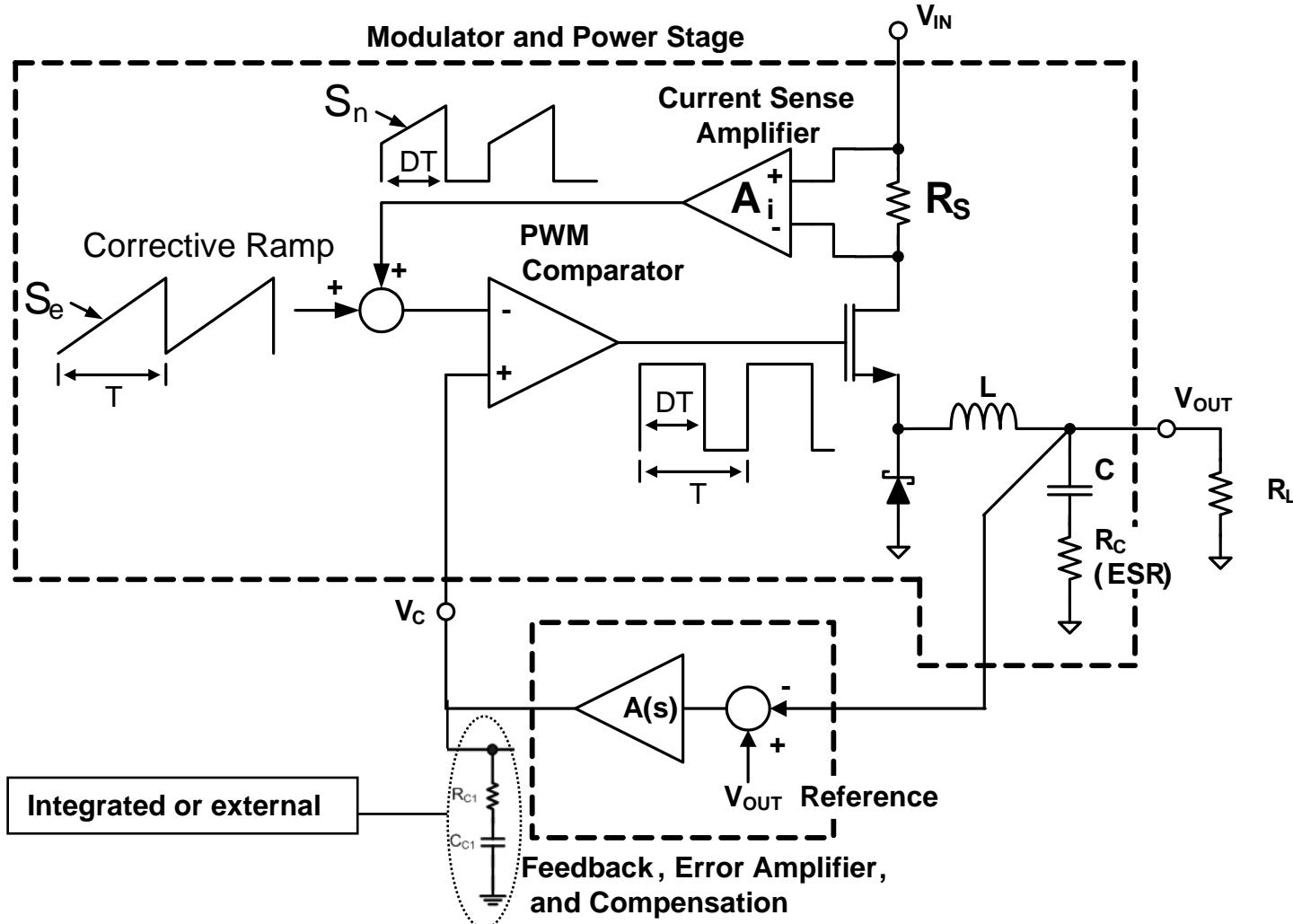
# Current-Mode Buck-Regulator Architecture




Peak-CMC architecture is used in most of Boost regulators and some Buck like LM28xx

# LM2840/41/42

## Tiny SOT-23 100-600mA Regulator
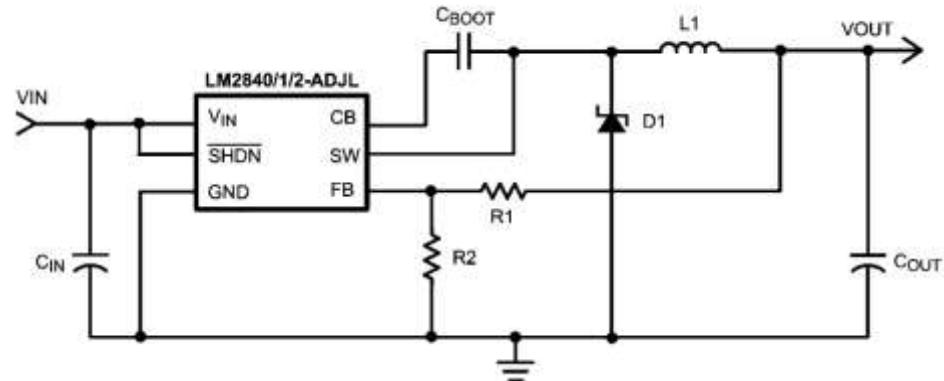
### Key Features

- Wide Vin range of **4.5V to 42V**
- 100mA / 300mA / 600mA** Output Current
- Internally compensated **current mode** control
- Fixed Operating Frequencies: 500kHz / 1.2MHz
- Adjustable output voltage down to 0.75V  $\pm 2\%$
- Precision Enable**
- Thermal shutdown
- Stable with Ceramic Capacitors
- Package: **SOT-23**
- Available in AEC-Q100 Grade 1 ( $T_{jmax}=125^\circ\text{C}$ )**



### Availability / Pricing

Order Code	Load Current [mA]	1K Web Price
LM2840	100	\$1.17
LM2841	300	\$1.29
LM2842	600	\$1.44

# TPS54360/ TPS54560 60V 3.5A DC-DC Regulator with EcoMode

## ОСОБЕННОСТИ

- Integrated 92mΩ High Side MOSFET
- Current Mode PWM with Light Load Eco-Mode™
- 146uA No-Load I<sub>q</sub>, 1uA Shutdown I<sub>q</sub>
- 100 kHz to 2.5 MHz Switching Frequency
- Synchronizes to External Clock
- 1% Accurate Feedback Voltage Reference
- -40 °C to +150 °C Operating Temperature

## ПРИМЕНЕНИЯ

- 24/36/48V Industrial Power Systems
- PLC, E-Meter, Security, Automation
- Automotive


Pin to pin  
compatibility across  
the family



HSOIC 8



SON10  
4mmx4mm


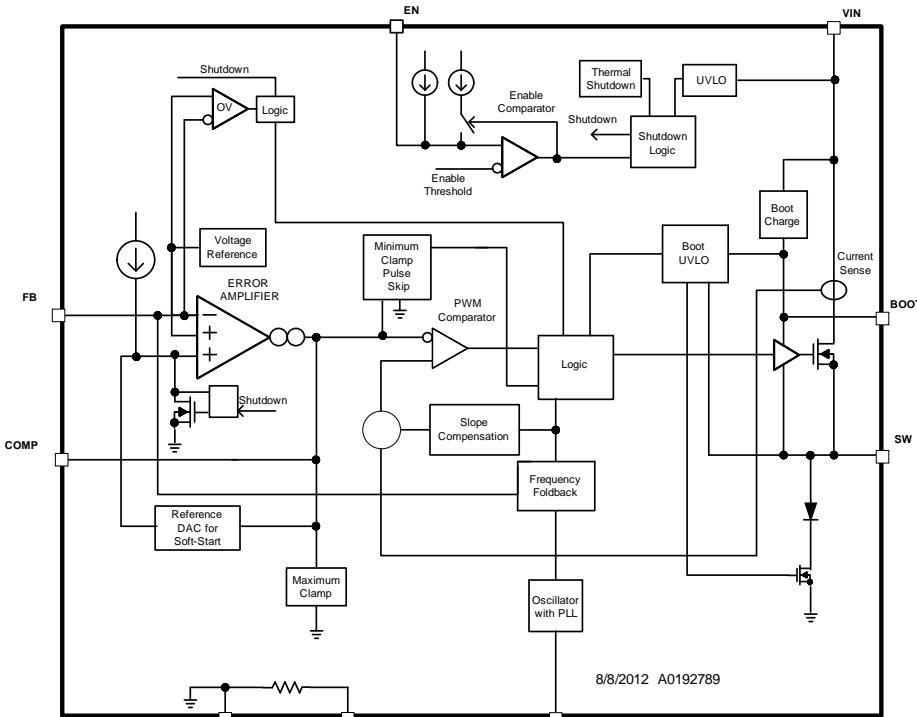


Part Number	I <sub>out</sub> (A)	V <sub>in</sub> (V)	Package	Release
TPS54360	3.5	4.5 - 60	HSOIC8	Now
TPS54340	3.5	4.5 - 42	HSOIC8	Now
TPS54560	5.0	4.5 - 60	HSOIC8	1Q13
TPS54540	5.0	4.5 - 42	HSOIC8	1Q13

# **Emulated Current Mode ECM Regulation**


**Большие соотношения Vin / Vout  
Устойчивость к помехам**

# Emulated Current Mode Waveforms

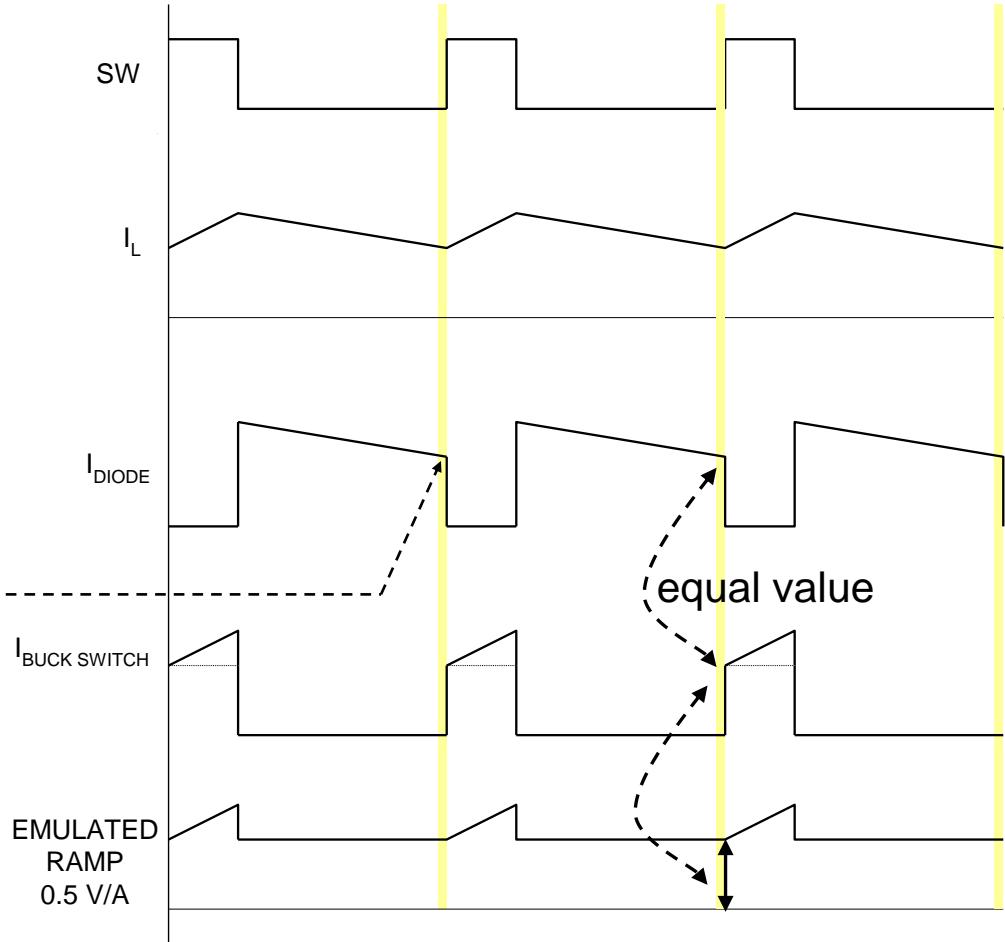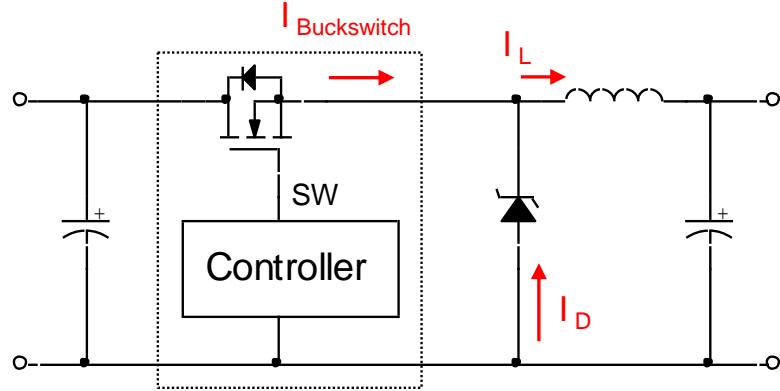

Due to the high input to output voltage ratios ON-times get too short to derive the regulation signal out of it.

# Emulated Current Mode Waveforms

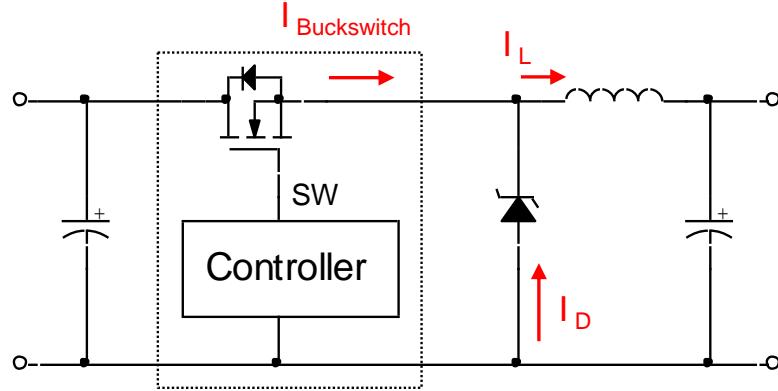


To emulate the ramping portion of the buck switch signal  $di/dt$  needs to be detected.


$$di/dt = (V_{in} - V_{out}) / L$$

Slope of Inductor Current  
 $di/dt = (V_{in} - V_{out}) / L$

Emulated Inductor Current

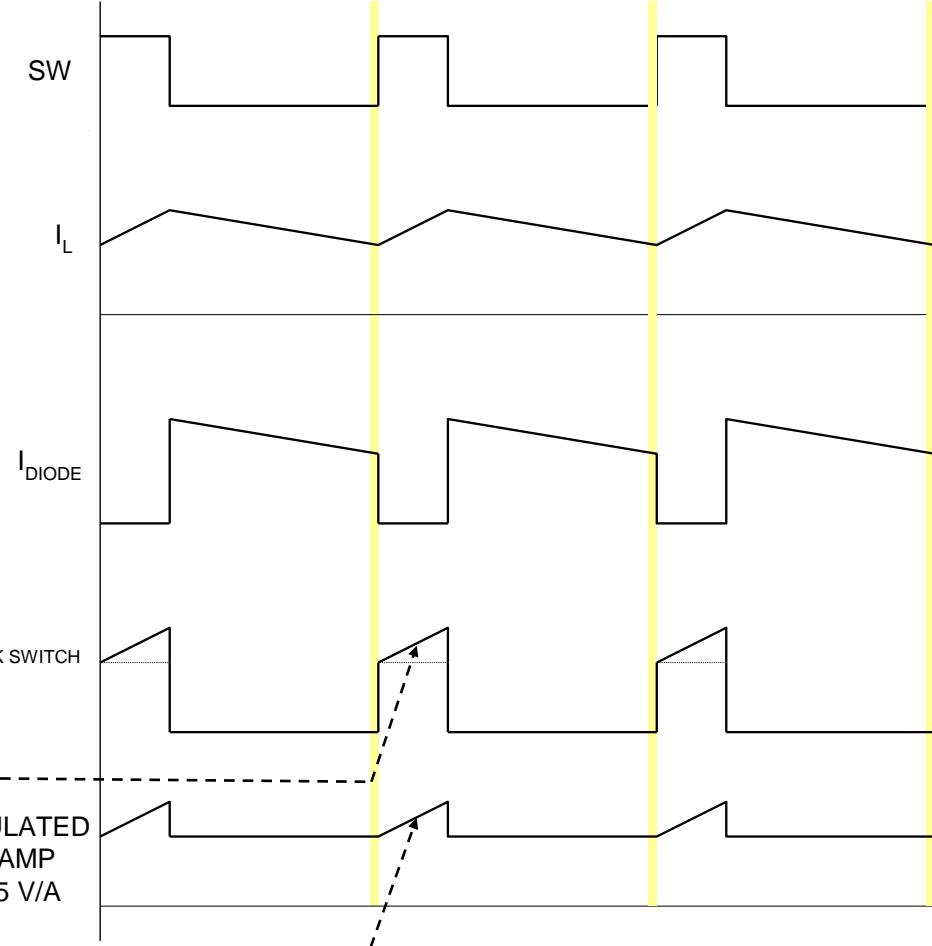


# Emulated-Current-Mode (ECM)

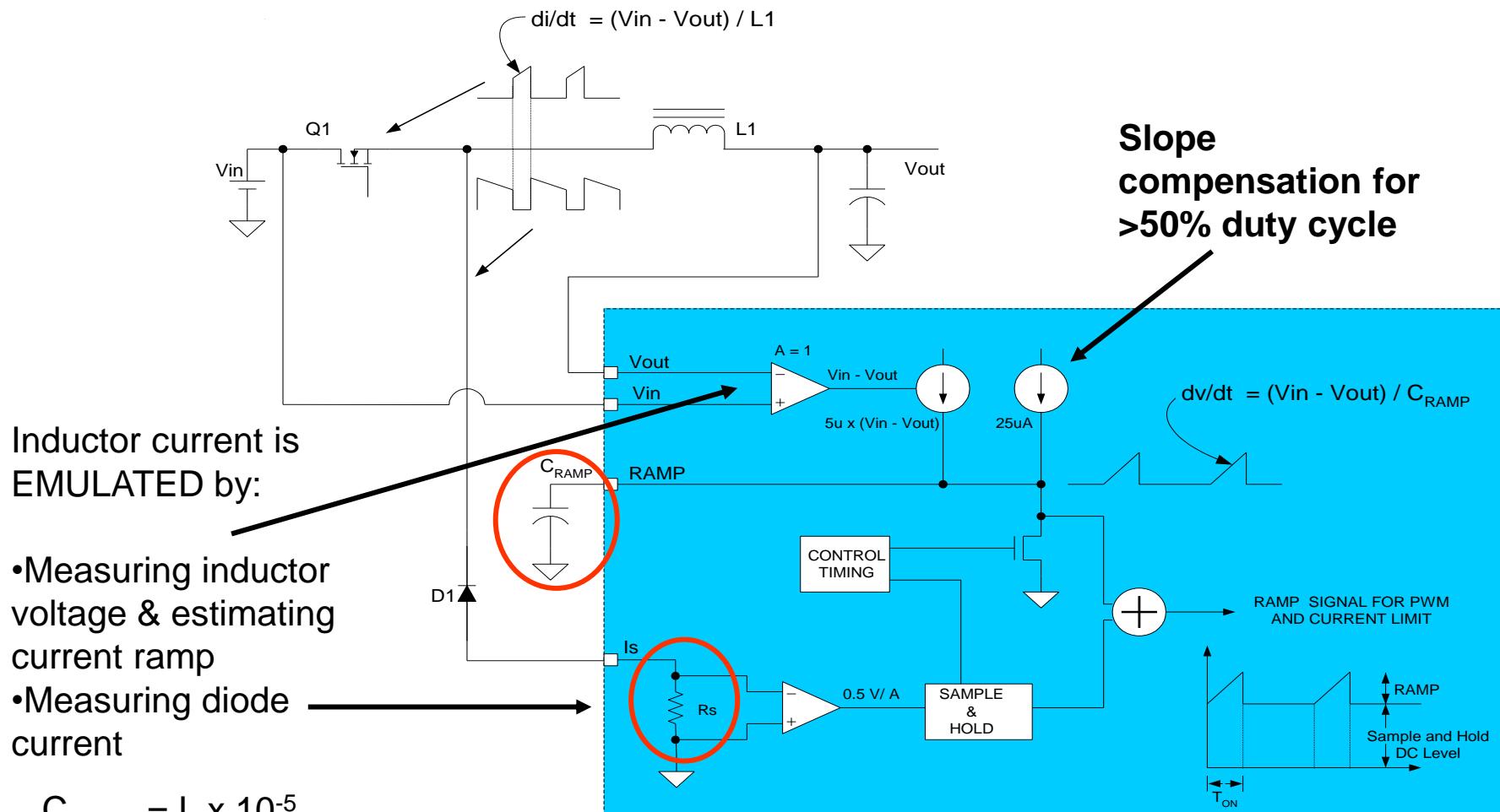

# Problem in normal Current Mode not a Problem in ECM !

Mosfet  
Current

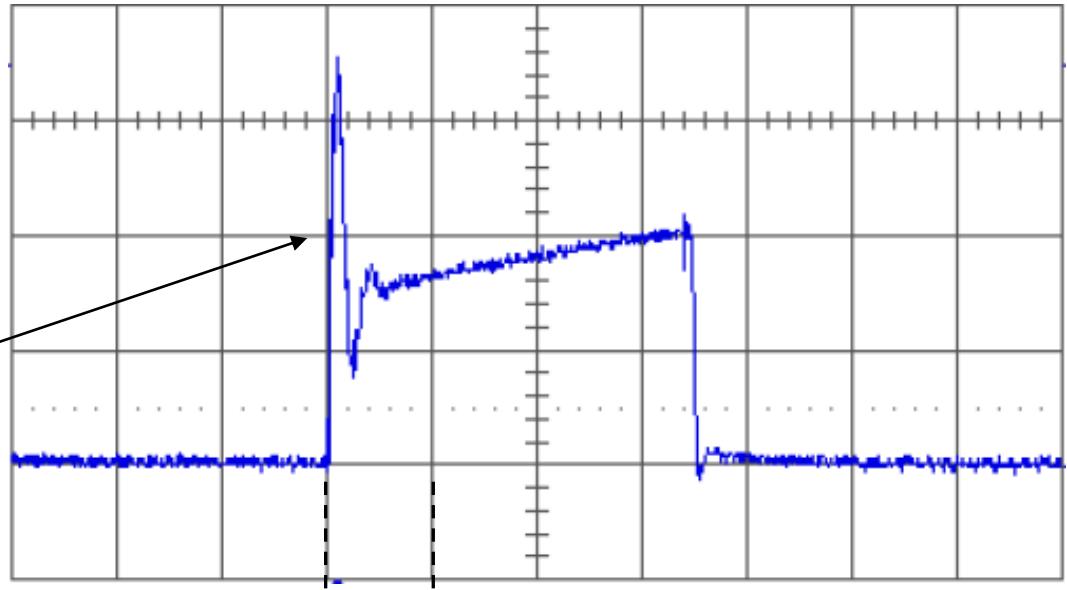


- Mosfet turns ON
- Leading edge spike, from reverse recovery current of diode


- Blanking time to avoid overdriving the PWM comparator

While current mode control provides better line (input voltage) regulation and better transient response, it is more susceptible to noise.
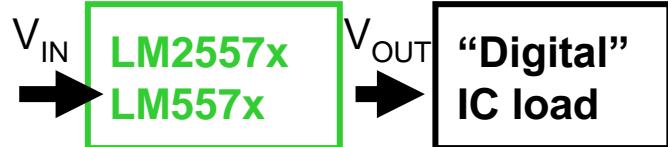
# Benefits of ECM vs.Voltage Mode: LM5576 Transient Response





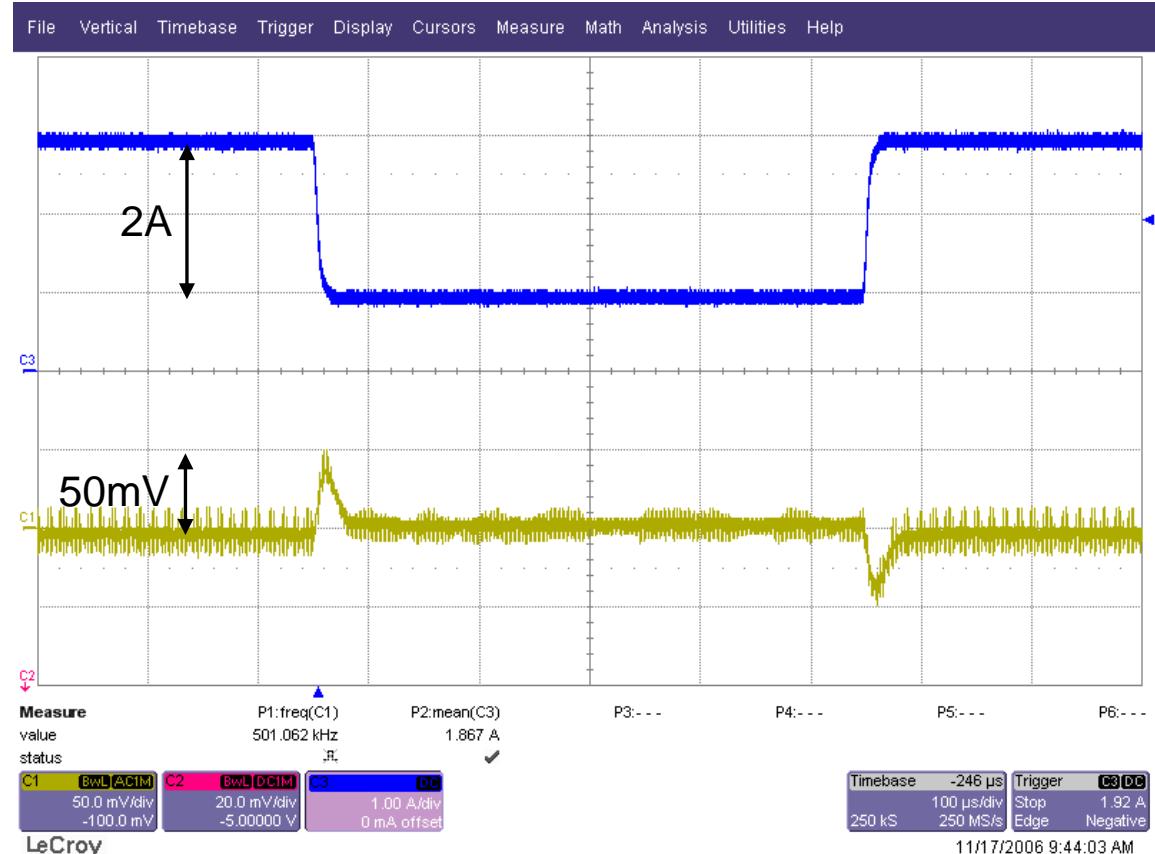- $V_{IN}=24V$
- $V_{OUT} = 5V$
- < 50mV output transient
- 1 to 3 Amp transient


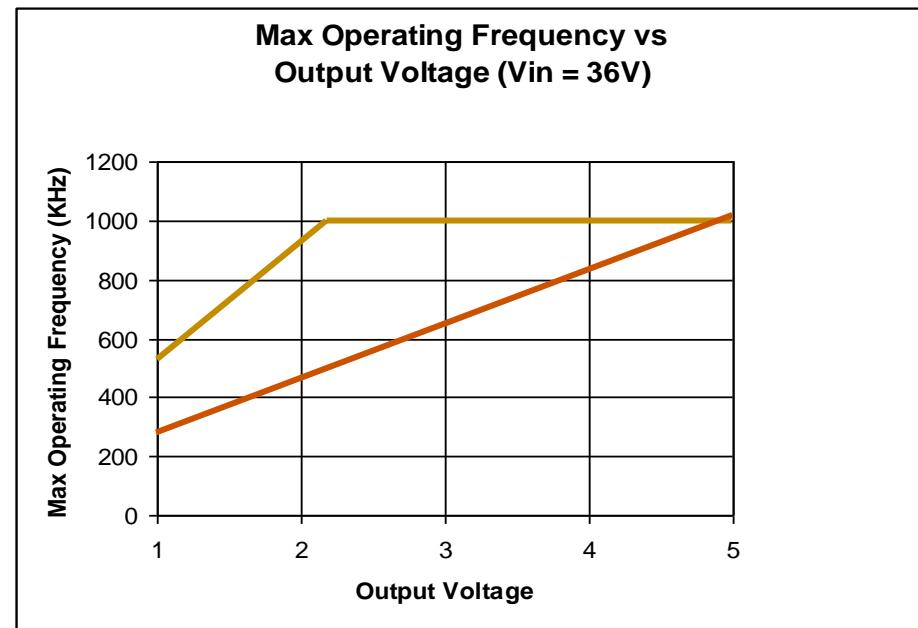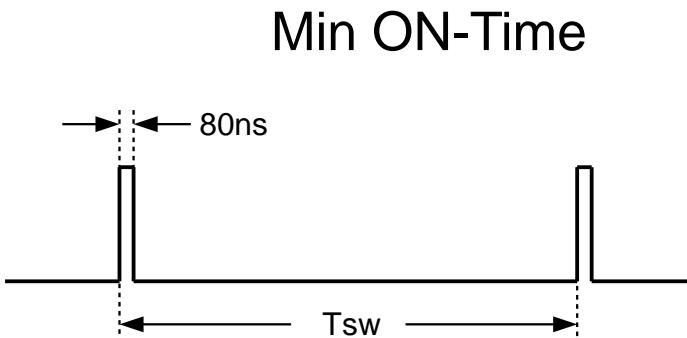
# Output Voltage vs. Operating Frequency


- The maximum operating frequency is a function of minimum ON-time & the input and output voltage.
- $f_{sw(max)} = (V_{OUT} + V_{diode}) / (t_{ON(MIN)} * V_{IN(max)})$



— Min ON time 80ns  
— Competitor 2.8MHz switcher, Min ON time 150ns
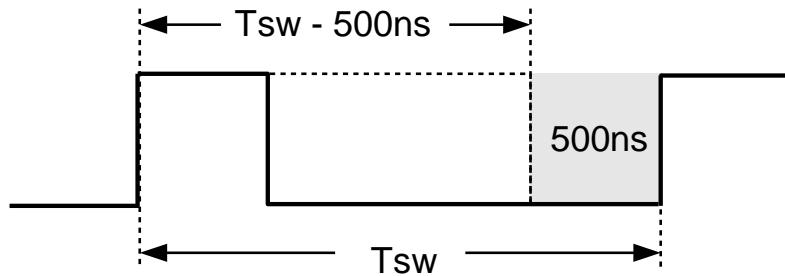
# Minimum Input Voltage vs. Operating Frequency

- Forced OFF-Time of 500ns
- To allow time for the sample & hold of the diode current
- The maximum duty cycle is limited for high frequency applications
- The minimum input voltage drop may be limited



$$V_{IN(min)} = (V_{OUT} + V_{diode}) / (1 - f_{sw}) * 500\text{ns}$$

Example1:  $V_{OUT}=5\text{V}$ ,  $f_{sw}=500\text{kHz}$ ,  $\rightarrow V_{IN(min)}=7\text{V}$


Example2:  $V_{OUT}=5\text{V}$ ,  $f_{sw}=800\text{kHz}$ ,  $\rightarrow V_{IN(min)}=9\text{V}$

# Надежная защита по току

- An additional benefit of ECM is “look-ahead current limiting” since the inductor current is measured prior to the buck switch on-time.

During high input voltage, extreme short-circuit conditions the buck switch will skip cycles if the inductor current does not decay below the current limit threshold.

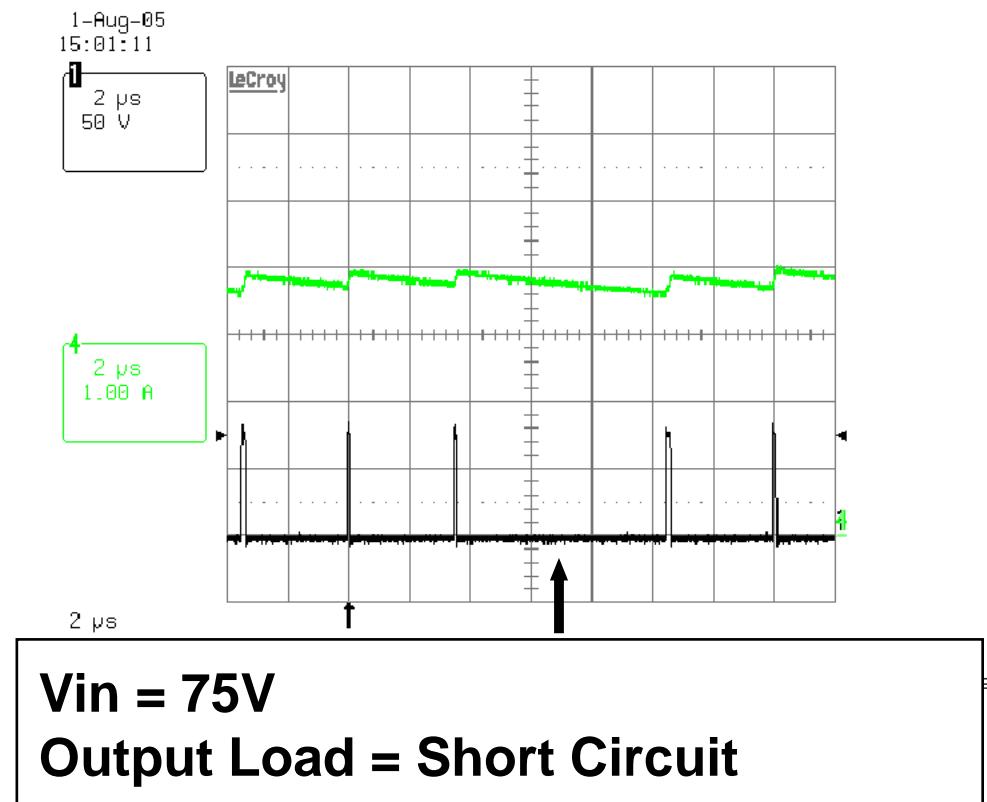Skipping cycles prevents the possibility of runaway inductor current.




# **SIMPLE SWITCHER®**

## **LM(2)557x Family**

# LM2557x / LM557x SIMPLE SWITCHER® Family
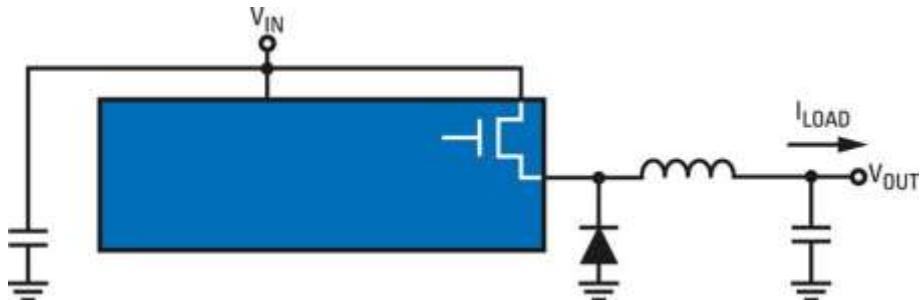
## Key Features

- Vin Range **6V to 42V / 75V**
- Current Outputs: **0.5A, 1.5A, 3.0A**
- Internally compensated **Emulated current mode** control for huge  $V_{IN}$  to  $V_{OUT}$  ratio
- Adjustable Output Voltages down to 1.225V
- **1.5%  $V_{OUT}$  Accuracy over full Temperature ( $T_j = -40^{\circ}C$  to  $+125^{\circ}C$ )**
- Enable pin
- **Adjustable Frequency (50kHz-1MHz / 500KHz)**
- **Frequency Sync (External or Master/Slave)**
- Adjustable Soft-Start
- Stable with Ceramic Capacitors
- **Available in AEC-Q100 Grade 1 ( $T_{jmax}=125^{\circ}C$ ) and Grade 0 ( $T_{jmax}=150^{\circ}C$ )**
- Packages:
  - TSSOP-16, TSSOP-16-EP, TSSOP-20-EP
  - **Bare Die version available**



## Availability / Pricing

Order Code	Load Current [A]	Vin [V]	1K Web Price
LM25574	0.5	42	\$1.48
LM5574	0.5	75	\$1.75
LM25575	1.5	42	\$1.76
LM5575	1.5	75	\$2.20
LM25576	3	42	\$2.40
LM5576	3	75	\$3.05

# **Заключение:**

# **Что для чего использовать?**

# Заключение: что для чего использовать?

## Voltage Mode

- Использовать, если необходима синхронизация или фиксированная частота.
- Для большой скважности предпочтительней, чем традиционный токовый режим.
- Максимальная простота реализации на м/к.
- LM2267x, LM21215, LM285x, TPS40007, TPS5430, TPS54610, TPS54310

## Voltage Mode (with Voltage Feed Forward)

- Если необходим актуально широкий диапазон рабочих напряжений.
- Автомобильная техника.
- TPS40170, TPS4005x, TPS56221, TPS40400

## Current Mode

- Если необходима синхронизация или фиксированная частота.
- Надежная защита, объединение по току. Промавтоматика.
- TPS54620, TPS54160, LM21305, TPS54618, TPS54331

## Emulated Current Mode

- Высокая устойчивость к помехам и переходным процессам в нагрузке.
- Высокая частота и скважность. Телеком UPS.
- LM557x, LM2557x, LM5005, LM5117, LM5116

# Заключение: что для чего использовать?

## Hysteretic

- Минимальная цена. Максимальная скорость реакции. Если частота не критична.
- LM3485, LM3475

## DCAP (Constant On Time)

- Лучшее соотношение качество/ цена. Малое количество компонентов.
- Оптимизирован под недорогие компоненты (medium ESR Cout).
- Adaptive COT: TPS51124, TPS51216, TPS53355, TPS53219
- COT: LM2500x, LM5006, LM5007/8/9, LM3100

## DCAP2 (Adaptive Constant On Time with Emulated Ripple Mode)

- Высокая устойчивость к помехам, переходным процессам в нагрузке, компоновке и разводке.
- Оптимизирован под керамические конденсаторы небольшой емкости.
- TPS54327/8, TPS54527/8, TPS53114, TPS5312x


## DCS (Direct Control w/ Seamless transition to Power Save Mode)

- Высокий КПД и динамические параметры.
- Портативные устройства.
- TPS62230, TPS62120/30/40/50


## **Приложение:**

**Выбор  
наиболее популярных  
компонентов  
по методам управления**

# Low Cost Step-Down DC/DC Converters

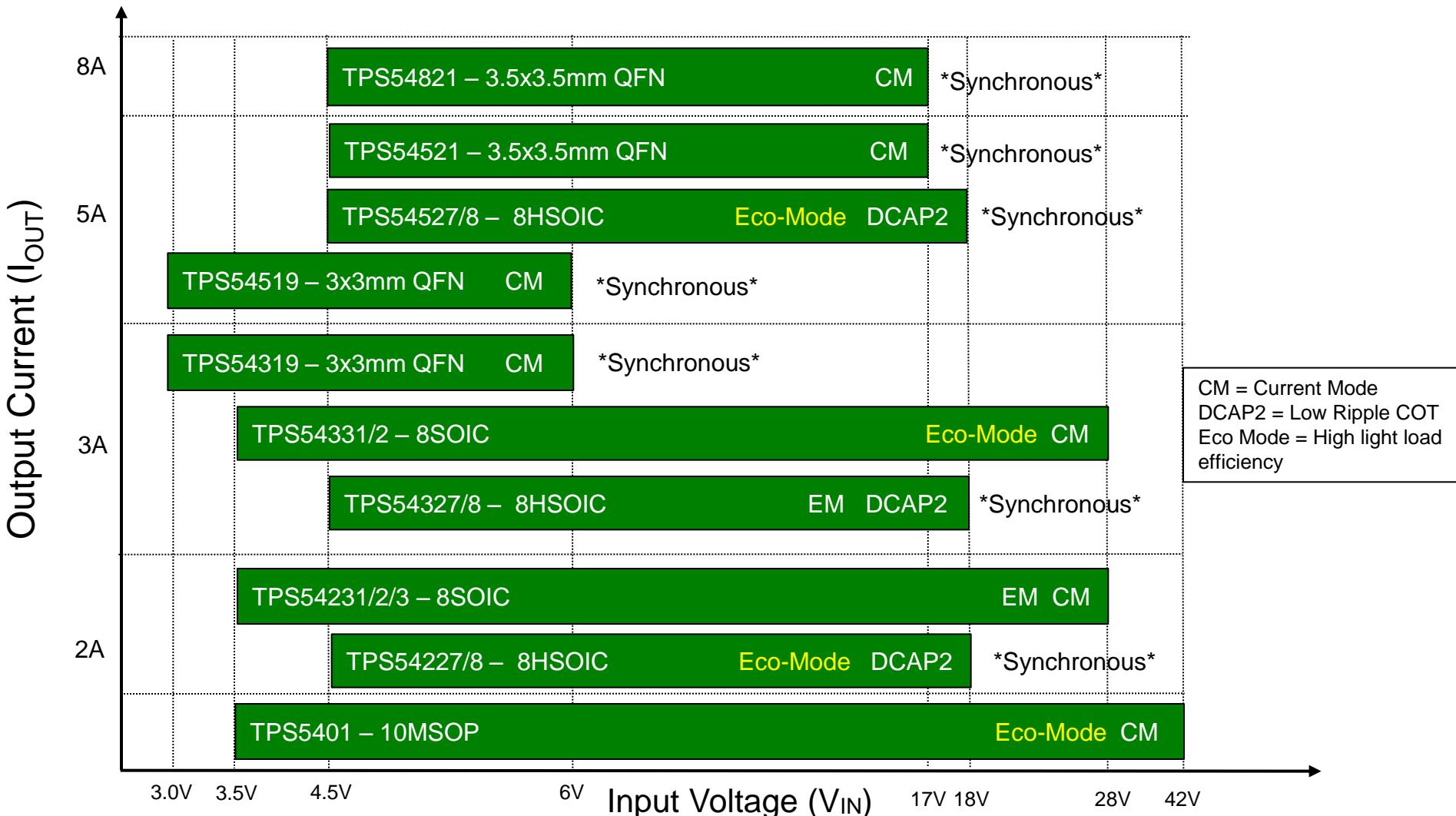

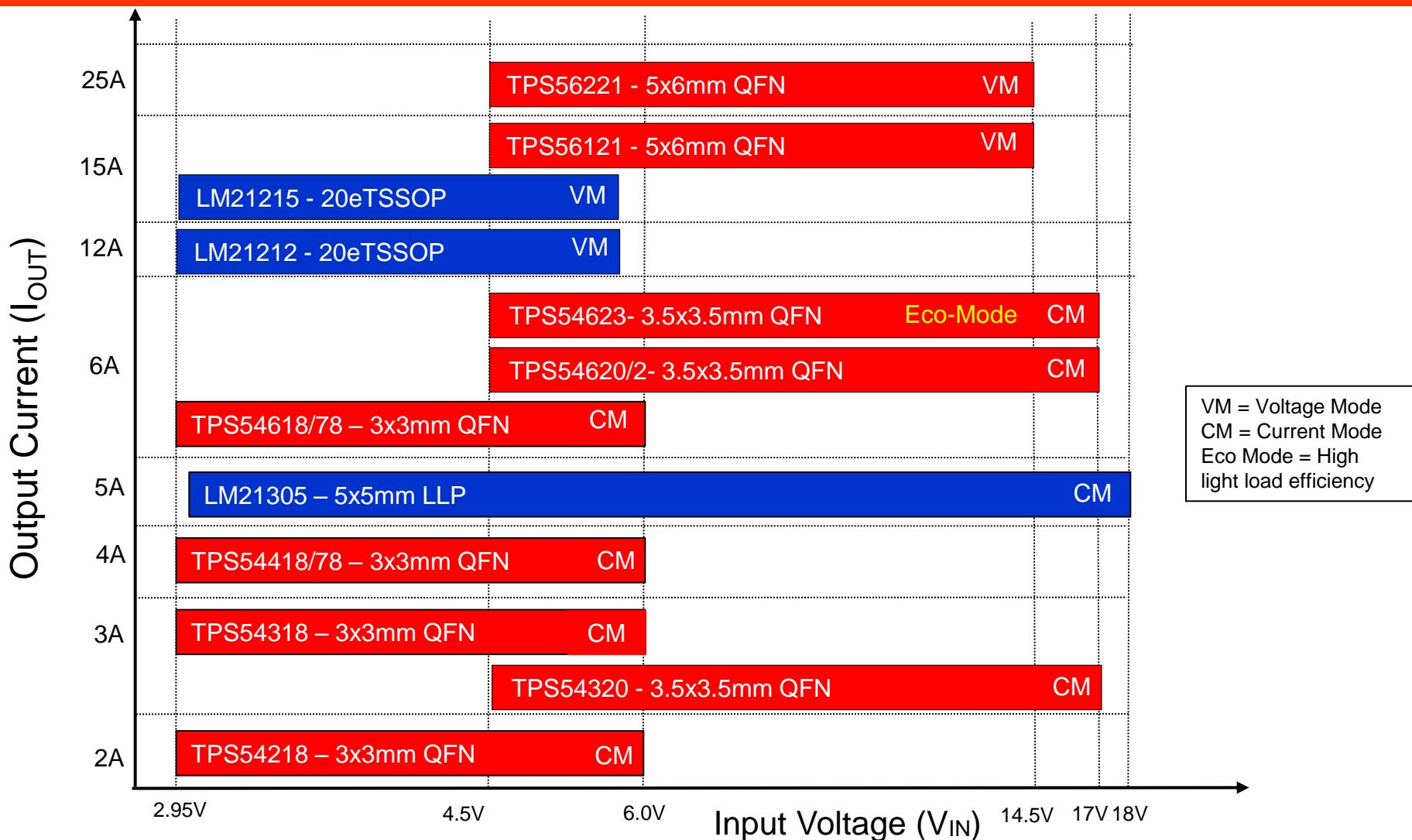
# Synchronous DC/DC Converters ( $V_{in} < 18V$ ) (Low/Mid Vin) for DSP / FPGA Power



# Industrial DC/DC Converters (Wide Vin)
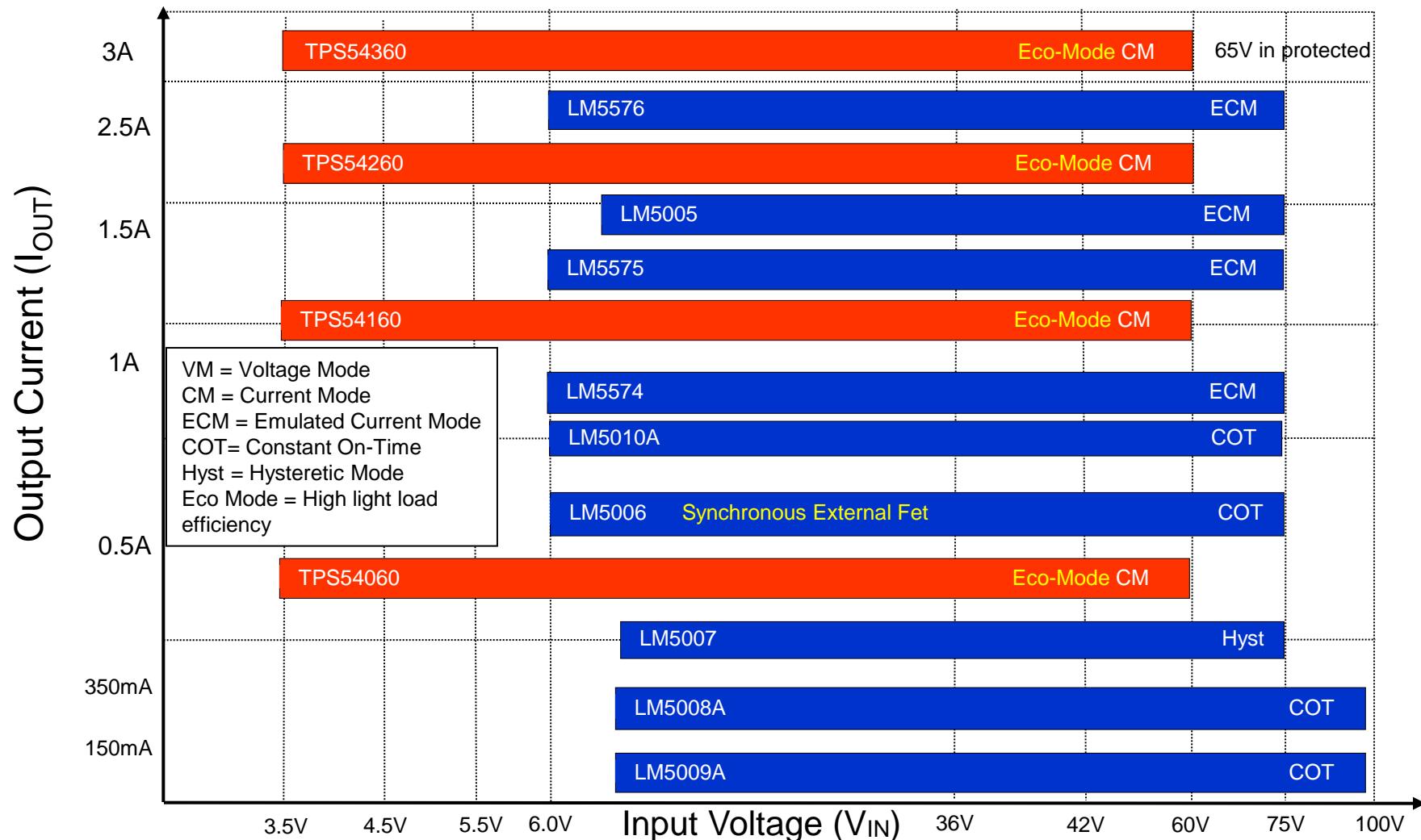
## Non-Synchronous Step-Down Converters > 42V Input



75V in max версии LM5XXX полностью совместимы с 42V версиями LM25XXX.

# Спасибо за внимание !